
Logic and Computer Design Fundamentals

Chapter 3 – Combinational Logic Design

Part 1 – Implementation Technology and Logic Design

Yueming Wang (王跃明)

ymingwang@zju.edu.cn

2018

College of Computer Science, Zhejiang University

Qiushi Academy for Advanced Studies, Zhejiang University

Overview


- **Part 1 – Implementation Technology and Logic Design**
 - **Some design topics and concepts**
 - **Design Procedure**
 - **Specification**
 - **Formulation**
 - **Optimization**
 - **Technology Mapping**
 - **Beginning Hierarchical Design**
 - **Technology Mapping**
 - **Verification**
 - **Manual**
 - **Simulation**

Overview (continued)

 - **Part 2 – Combinational Logic**
 - **Functions and functional blocks**
 - **Rudimentary logic functions**
 - **Decoding using Decoders**
 - **Implementing Combinational Functions with Decoders**
 - **Encoding using Encoders**
 - **Selecting using Multiplexers**
 - **Implementing Combinational Functions with Multiplexers**

Combinational Circuits

- A combinational logic circuit has:
 - A set of m Boolean inputs,
 - A set of n Boolean outputs, and
 - n switching functions, each mapping the 2^m input combinations to an output such that the current output depends only on the current input values



Integrated Circuits

- **Integrated circuit (informally, a “chip”) is a semiconductor crystal (most often silicon) containing the electronic components for the digital gates and storage elements which are interconnected on the chip.**
- **Terminology - Levels of chip integration**
 - *SSI (small-scale integrated)* - fewer than 10 gates
 - *MSI (medium-scale integrated)* - 10 to 100 gates
 - *LSI (large-scale integrated)* - 100 to thousands of gates
 - *VLSI (very large-scale integrated)* - thousands to 100s of millions of gates

Technology Parameters

- **Specific gate implementation technologies are characterized by the following parameters:**
 - ***Fan-in*** – the number of inputs available on a gate
 - ***Fan-out*** – the number of standard loads driven by a gate output
 - ***Logic Levels*** – the signal value ranges for 1 and 0 on the inputs and 1 and 0 on the outputs (see Figure 1-1)
 - ***Noise Margin*** – the maximum external noise voltage superimposed on a normal input value that will not cause an undesirable change in the circuit output
 - ***Cost for a gate*** - a measure of the contribution by the gate to the cost of the integrated circuit
 - ***Propagation Delay*** – The time required for a change in the value of a signal to propagate from an input to an output
 - ***Power Dissipation*** – the amount of power drawn from the power supply and consumed by the gate

Fan-out

- **Fan-out can be defined in terms of a standard load**
 - **Example: 1 standard load equals the load contributed by the input of 1 inverter.**
 - ***Transition time* -the time required for the gate output to change from H to L, t_{HL} , or from L to H, t_{LH}**
 - **The *maximum fan-out* that can be driven by a gate is the number of standard loads the gate can drive without exceeding its specified *maximum transition time***


Cost

- **In an integrated circuit:**
 - The cost of a gate is proportional to the chip area occupied by the gate
 - The gate area is roughly proportional to the number and size of the transistors and the amount of wiring connecting them
 - Ignoring the wiring area, the gate area is roughly proportional to the gate input count
 - So gate input count is a rough measure of gate cost
- **If the actual chip layout area occupied by the gate is known, it is a far more accurate measure**

Propagation Delay

- *Propagation delay* is the time for a change on an input of a gate to propagate to the output.
- Delay is usually measured at the 50% point with respect to the H and L output voltage levels.
- High-to-low (t_{PHL}) and low-to-high (t_{PLH}) output signal changes may have different propagation delays.
- High-to-low (HL) and low-to-high (LH) transitions are defined with respect to the output, not the input.
- An HL input transition causes:
 - an LH output transition if the gate inverts and
 - an HL output transition if the gate does not invert.


Propagation Delay (continued)

 

- Propagation delays measured at the midpoint between the L and H values

Propagation Delay Example

 
- Find t_{PHL} , t_{PLH} and t_{pd} for the signals given



Delay Models

- ***Transport delay*** - a change in the output in response to a change on the inputs occurs after a fixed specified delay
- ***Inertial delay*** - similar to transport delay, except that if the input changes such that the output is to change twice in a time interval less than the *rejection time*, the output changes do not occur. Models typical electronic circuit behavior, namely, rejects narrow “pulses” on the outputs




Delay Model Example

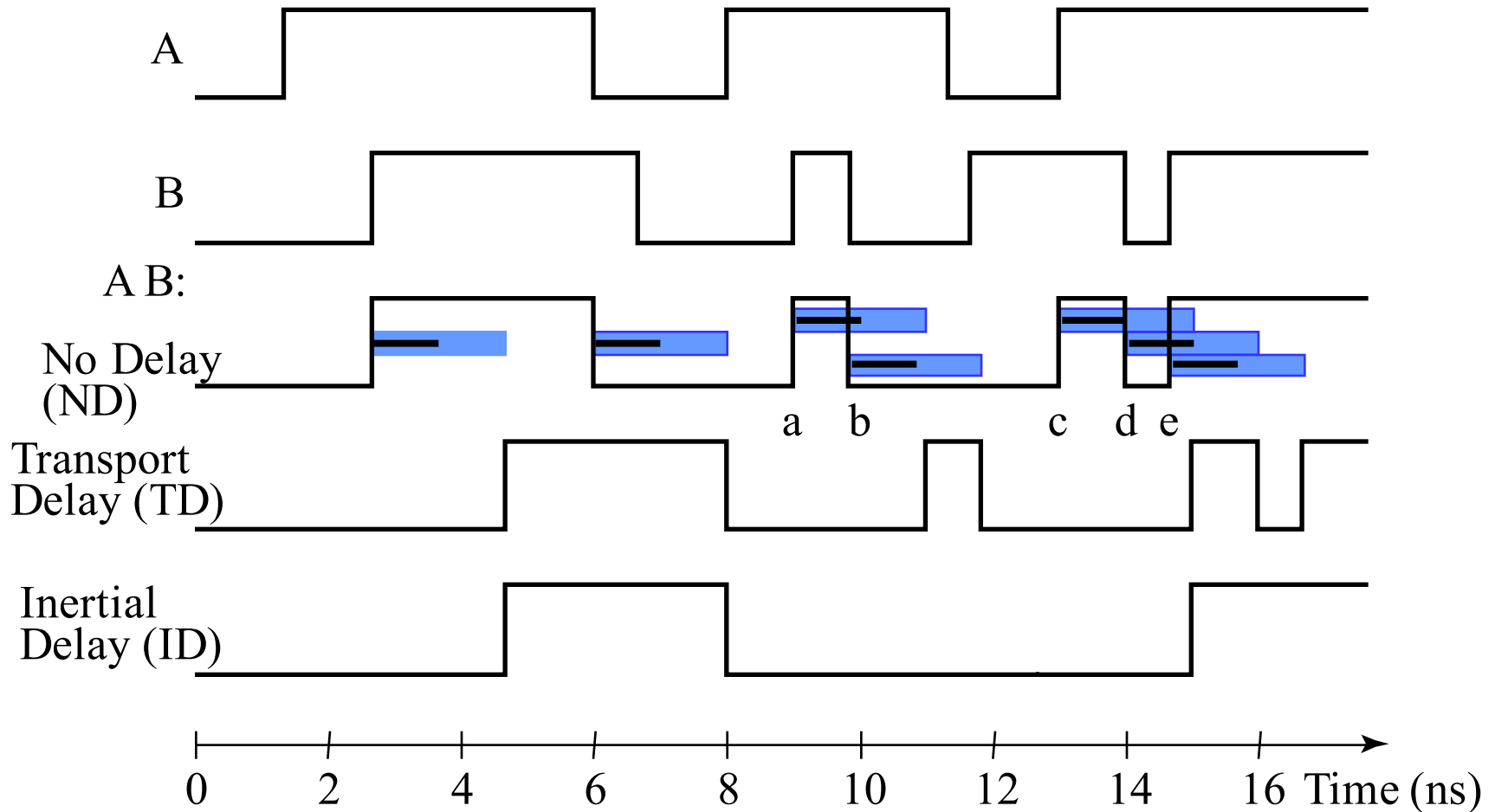

Propagation Delay = 2.0 ns Rejection Time = 1.0 ns

Circuit Delay

   - Suppose gates with delay n ns are represented for $n = 0.2$ ns, $n = 0.4$ ns, $n = 0.5$ ns, respectively:





Circuit Delay

- Consider a simple 2-input multiplexer:

- With function:

  - $Y = A$ for $S = 0$
- $Y = B$ for $S = 1$



- “Glitch” is due to delay of inverter

Fan-out and Delay

- **The fan-out loading a gate's output affects the gate's propagation delay**
- **Example:**
 - **One realistic equation for t_{pd} for a NAND gate with 4 inputs is:**
$$t_{pd} = 0.07 + 0.021 \text{ SL ns}$$
 - **SL is the number of standard loads the gate is driving, i. e., its fan-out in standard loads**
 - **For $\text{SL} = 4.5$, $t_{pd} = 0.165 \text{ ns}$**
- **If this effect is considered, the delay of a gate in a circuit takes on different values depending on the circuit load on its output.**

Cost/Performance Tradeoffs

- **Gate-Level Example:**
 - **NAND gate G with 20 standard loads on its output has a delay of 0.45 ns and has a normalized cost of 2.0**
 - **A buffer H has a normalized cost of 1.5. The NAND gate driving the buffer with 20 standard loads gives a total delay of 0.33 ns**
 - **In which of the following cases should the buffer be added?**
 - 1. The cost of this portion of the circuit cannot be more than 2.5**
 - 2. The delay of this portion of the circuit cannot be more than 0.40 ns**
 - 3. The delay of this portion of the circuit must be less than 0.40 ns and the cost less than 3.0**
- **Tradeoffs can also be accomplished much higher in the design hierarchy**
- **Constraints on cost and performance have a major role in making tradeoffs**

Design Procedure

1. Specification

- Write a specification for the circuit if one is not already available

2. Formulation

- Derive a truth table or initial Boolean equations that define the required relationships between the inputs and outputs, if not in the specification
- Apply hierarchical design if appropriate

3. Optimization

- Apply 2-level and multiple-level optimization
- Draw a logic diagram or provide a netlist for the resulting circuit using ANDs, ORs, and inverters

Design Procedure

4. Technology Mapping

- Map the logic diagram or netlist to the implementation technology selected

5. Verification

- Verify the correctness of the final design manually or using simulation

Design Example

1. Specification

- BCD to Excess-3 code converter
- Transforms BCD code for the decimal digits to Excess-3 code for the decimal digits
- BCD code words for digits 0 through 9: 4-bit patterns 0000 to 1001, respectively
- Excess-3 code words for digits 0 through 9: 4-bit patterns consisting of 3 (binary 0011) added to each BCD code word
- Implementation:
 - multiple-level circuit
 - NAND gates (including inverters)

Design Example (continued)

2. Formulation

- Conversion of 4-bit codes can be most easily formulated by a truth table

- Variables

- BCD:

A,B,C,D

- Variables

- Excess-3

W,X,Y,Z

- Don't Cares

- BCD 1010

to 1111

Input BCD A B C D	Output Excess-3 W X Y Z
0 0 0 0	0 0 1 1
0 0 0 1	0 1 0 0
0 0 1 0	0 1 0 1
0 0 1 1	0 1 1 0
0 1 0 0	0 1 1 1
0 1 0 1	1 0 0 0
0 1 1 0	1 0 0 1
0 1 1 1	1 0 1 0
1 0 0 0	1 0 1 1
1 0 0 1	1 1 0 0

Design Example (continued)

3. Optimization


a. 2-level using K-maps

$$W = A + BC + BD$$

$$X = \bar{B}C + \bar{B}D + B\bar{C}\bar{D}$$

$$Y = CD + \bar{C}\bar{D}$$

$$Z = \bar{D}$$

 

Design Example (continued)

3. Optimization (continued)

b. Multiple-level using transformations

$$W = A + BC + BD$$

$$X = \overline{B}C + \overline{B}D + B\overline{C}\overline{D}$$

$$Y = CD + \overline{C}\overline{D}$$

$$Z = \overline{D}$$

$$G = 7 + 10 + 6 + 0 = 23$$

- Perform extraction, finding factor:

$$T_1 = C + D$$

$$W = A + BT_1$$

$$X = \overline{B}T_1 + B\overline{C}\overline{D}$$

$$Y = CD + \overline{C}\overline{D}$$

$$Z = \overline{D}$$

$$G = 2 + 4 + 7 + 6 + 0 = 19$$

Design Example (continued)

3. Optimization (continued)

b. Multiple-level using transformations

$$T_1 = C + D$$

$$W = A + BT_1$$

$$X = \overline{B}T_1 + B\overline{C}\overline{D}$$

$$Y = CD + \overline{C}\overline{D}$$

$$Z = \overline{D}$$

$$G = 19$$

- An additional extraction not shown in the text since it uses a Boolean transformation: ($\overline{C}\overline{D} = \overline{C + D} = \overline{T}_1$):

$$W = A + BT_1$$

$$X = \overline{B}T_1 + B\overline{T}_1$$

$$Y = CD + \overline{T}_1$$


$$Z = \overline{D}$$

$$G = 2 + 4 + 6 + 4 + 0 = 16!$$

Design Example (continued)

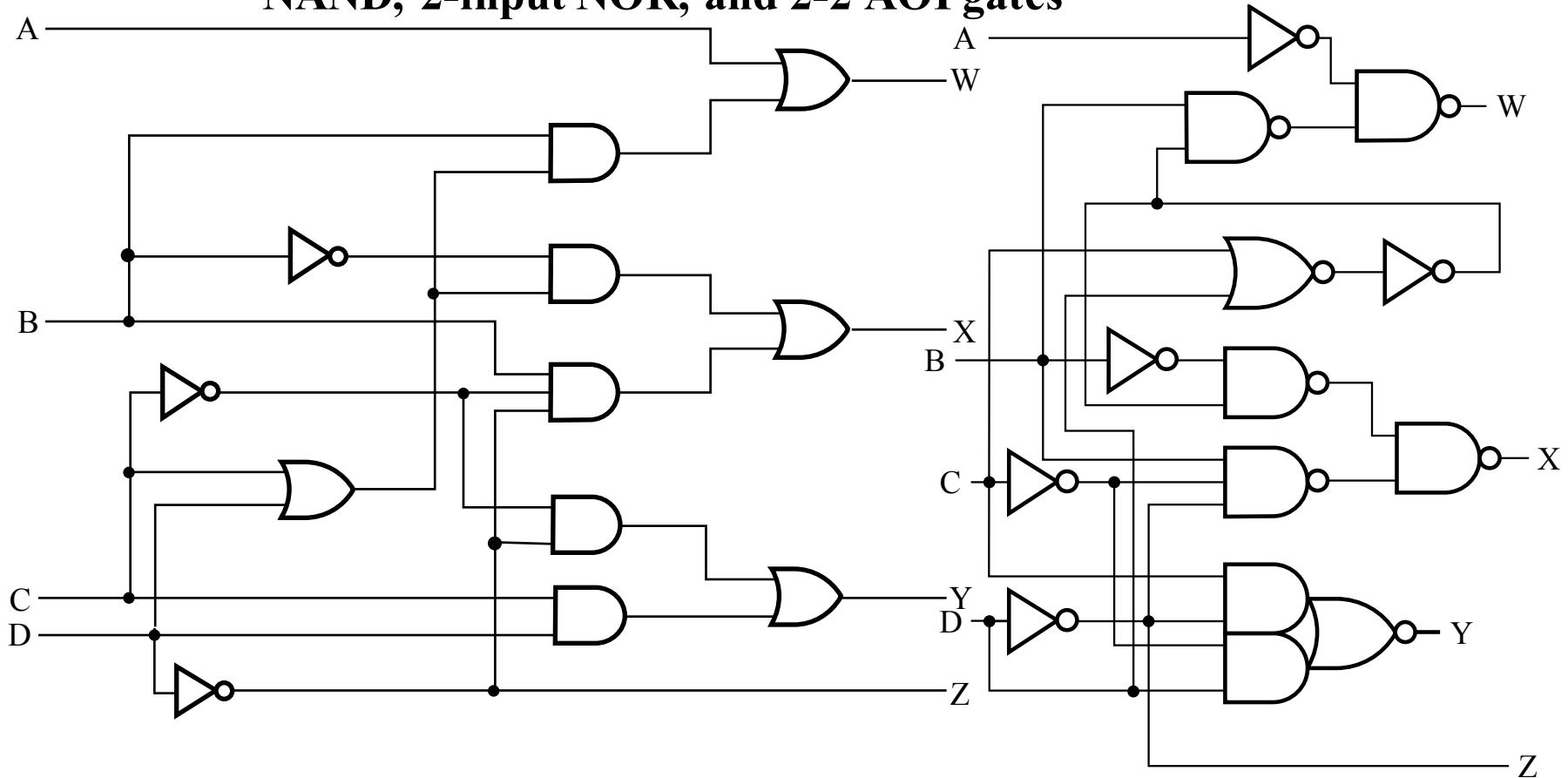4. Technology Mapping





- Mapping with a library containing inverters and 2-input NAND, 2-input NOR, and 2-2 AOI gates



Beginning Hierarchical Design

- To control the complexity of the function mapping inputs to outputs:
 - Decompose the function into smaller pieces called *blocks*
 - Decompose each block's function into smaller blocks, repeating as necessary until all blocks are small enough
 - Any block not decomposed is called a *primitive block*
 - The collection of all blocks including the decomposed ones is a *hierarchy*
- Example: (next slide)

Hierarchy for Parity Tree Example

  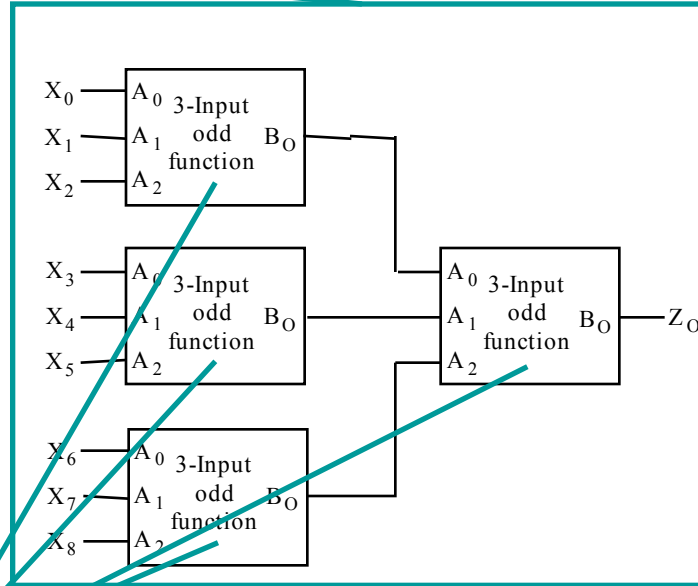 

- 9-input parity tree
 - Top Level: 9 inputs, one output
 - 2nd Level: Four 3-bit odd parity trees in two levels
 - 3rd Level: Two 2-bit exclusive-OR functions
 - Primitives: Four 2-input NAND gates
 - Design requires $4 \times 2 \times 4 = 32$ 2-input NAND gates

Reusable Functions

- **Whenever possible, we try to decompose a complex design into common, *reusable* function blocks**
- **These blocks are**
 - **verified and well-documented**
 - **placed in libraries for future use**

Top-Down versus Bottom-Up

- A *top-down design* proceeds from an abstract, high-level specification to a more and more detailed design by decomposition and successive refinement
- A *bottom-up design* starts with detailed primitive blocks and combines them into larger and more complex functional blocks
- Design usually proceeds top-down to known building blocks ranging from complete CPUs to primitive logic gates or electronic components.
- Much of the material in this chapter is devoted to learning about combinational blocks used in top-down design.

Technology Mapping

- **Mapping Procedures**
 - **To NAND gates**
 - **To NOR gates**
 - **Mapping to multiple types of logic blocks in covered in the reading supplement:
Advanced Technology Mapping.**

Mapping to NAND gates

■ Assumptions:


- Gate loading and delay are ignored
- Cell library contains an inverter and n -input NAND gates, $n = 2, 3, \dots$
- An AND, OR, inverter schematic for the circuit is available

■ The mapping is accomplished by:

- Replacing AND and OR symbols,
- Pushing inverters through circuit fan-out points, and
- Canceling inverter pairs


NAND Mapping Algorithm

1. Replace ANDs and ORs:

 


2. Repeat the three steps of actions until there is at most one inverter between :

 
- a. A circuit input or driving NAND gate output, and
- b. The attached NAND gate inputs.




NAND Mapping Example

 


(a)

 

(b)

 

(c)

 

(d)

Mapping to NOR gates

■ Assumptions:


- Gate loading and delay are ignored
- Cell library contains an inverter and n -input NOR gates, $n = 2, 3, \dots$
- An AND, OR, inverter schematic for the circuit is available

■ The mapping is accomplished by:

- Replacing AND and OR symbols,
- Pushing inverters through circuit fan-out points, and
- Canceling inverter pairs


NOR Mapping Algorithm

1. Replace ANDs and ORs:

 

2. Repeat the three steps of actions until there is at most one inverter between :

 - a. A circuit input or driving NAND gate output, and
- b. The attached NAND gate inputs.





Verification

- **Verification - show that the final circuit designed implements the original specification**
- **Simple specifications are:**
 - truth tables
 - Boolean equations
 - HDL code
- **If the above result from formulation and are not the original specification, it is critical that the formulation process be flawless for the verification to be valid!**

Basic Verification Methods

■ Manual Logic Analysis

- Find the truth table or Boolean equations for the final circuit
- Compare the final circuit truth table with the specified truth table, or
- Show that the Boolean equations for the final circuit are equal to the specified Boolean equations

■ Simulation

- Simulate the final circuit (or its netlist, possibly written as an HDL) and the specified truth table, equations, or HDL description using test input values that fully validate correctness.
- The obvious test for a combinational circuit is application of all possible “care” input combinations from the specification

Verification Example: Manual Analysis

- **BCD-to-Excess 3 Code Converter**
 - Find the SOP Boolean equations from the final circuit.
 - Find the truth table from these equations
 - Compare to the formulation truth table

- **Finding the Boolean Equations:**

$$T_1 = \overline{\overline{C} + \overline{D}} = C + D$$

$$W = \overline{\overline{A} (\overline{T_1} \overline{B})} = A + B T_1$$

$$X = (T_1 B) (B \overline{C} \overline{D}) = \overline{B} T_1 + B \overline{C} \overline{D}$$

$$Y = \overline{C \overline{D} + \overline{C} D} = CD + \overline{C} \overline{D}$$

Verification Example: Manual Analysis

- Find the circuit truth table from the equations and compare to specification truth table:

Input BCD A B C D	Output Excess-3 WXYZ
0 0 0 0	0 0 1 1
0 0 0 1	0 1 0 0
0 0 1 0	0 1 0 1
0 0 1 1	0 1 1 0
0 1 0 0	0 1 1 1
0 1 0 1	1 0 0 0
0 1 1 0	1 0 0 1
0 1 1 1	1 0 1 0
1 0 0 0	1 0 1 1
1 0 0 1	1 0 1 1


The tables match!

Verification Example: Simulation

- **Simulation procedure:**
 - **Use a schematic editor or text editor to enter a gate level representation of the final circuit**
 - **Use a waveform editor or text editor to enter a test consisting of a sequence of input combinations to be applied to the circuit**
 - **This test should guarantee the correctness of the circuit if the simulated responses to it are correct**
 - **Short of applying all possible “care” input combinations, generation of such a test can be difficult**


Verification Example: Simulation

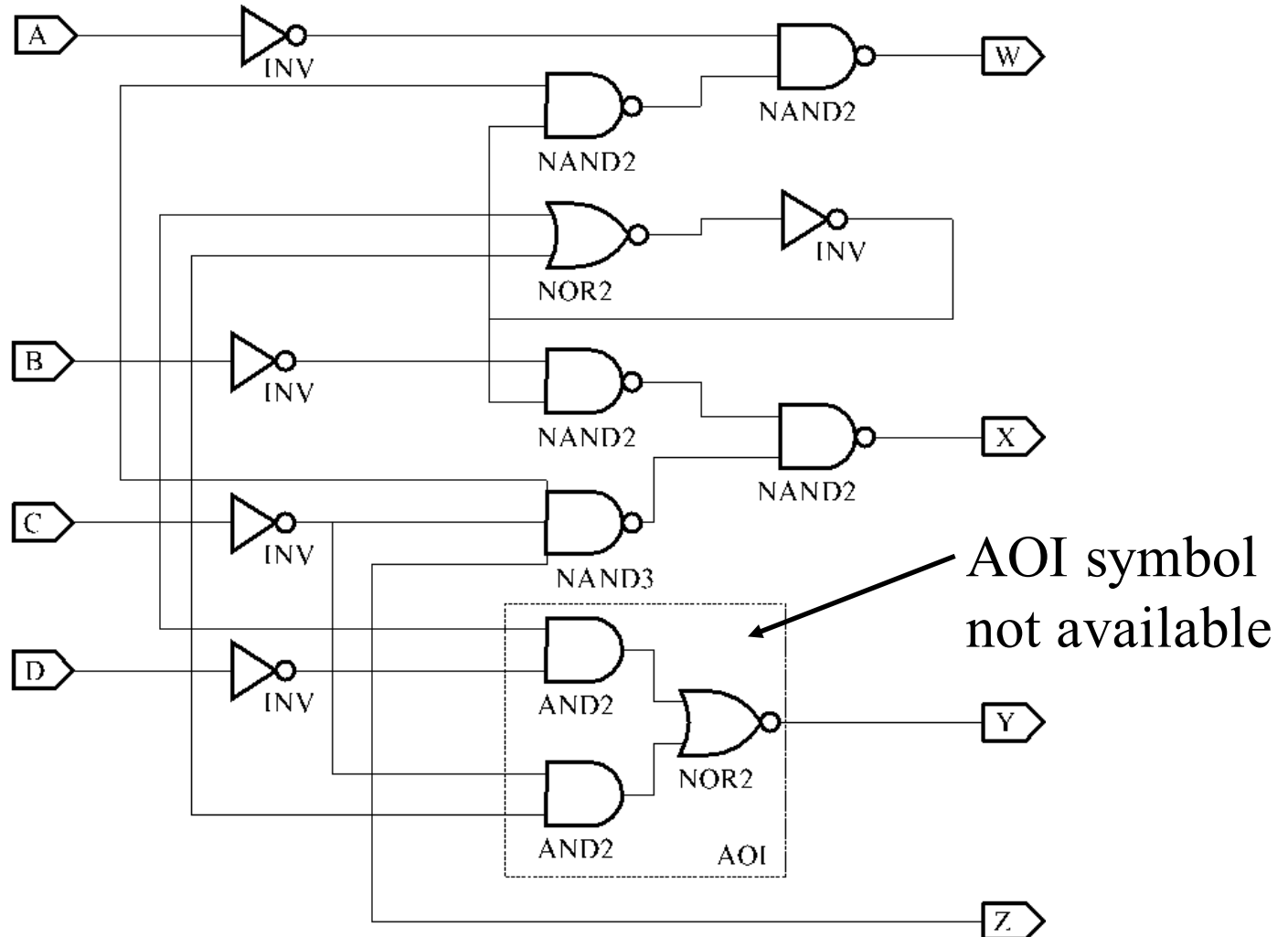- Enter BCD-to-Excess-3 Code Converter Circuit Schematic



Verification Example: Simulation

 
- Enter waveform that applies all possible input combinations:



- Are all BCD input combinations present? (Low is a 0 and high is a one)

Verification Example: Simulation

 - **Run the simulation of the circuit for 120 ns**



- **Do the simulation output combinations match the original truth table?**

Assignment

- 3-7, 3-8, 3-11, 3-13, 3-14, 3-16, 3-27, 3-28, 3-29, 3-37, 3-44, 3-47, 3-50, 3-51, 3-52, 3-59