

Logic and Computer Design Fundamentals

Chapter 2 – Combinational Logic Circuits

Part I – Gate Circuits and Boolean Equations

Yueming Wang (王跃明)

ymingwang@zju.edu.cn

2018

College of Computer Science, Zhejiang University

Qiushi Academy for Advanced Studies, Zhejiang University

Overview

- **Part 1 – Gate Circuits and Boolean Equations**
 - **Binary Logic and Gates**
 - **Boolean Algebra**
 - **Standard Forms**
- **Part 2 – Circuit Optimization**
 - **Two-Level Optimization**
 - **Map Manipulation**
 - **Practical Optimization (Espresso)**
 - **Multi-Level Circuit Optimization**
- **Part 3 – Additional Gates and Circuits**
 - **Other Gate Types**
 - **Exclusive-OR Operator and Gates**
 - **High-Impedance Outputs**

Binary Logic and Gates

➤ Binary Logic

– Binary variables

- take on one of two values, 1 and 0
- A, B, y, z, or X_1 for now, RESET, START_IT, or ADD1 later

– Logical operators

- operate on binary values and binary variables.
- Basic logical operators are the logic functions AND, OR and NOT.

➤ Logic gates

- implement logic functions.
- Basic circuits

➤ Boolean Algebra

- a useful mathematical system for specifying and transforming logic functions.

➤ We study Boolean algebra as a foundation for designing and analyzing digital systems!

Logical Operations

- **The three basic logical operations are:**
 - **AND**
 - **OR**
 - **NOT**
- **AND is denoted by a dot (\cdot), \times , \wedge , or even none.**
- **OR is denoted by a plus ($+$) or \vee , $.$**
- **NOT is denoted by an overbar ($\bar{}$), a single quote mark ($'$) after, or (\sim) before the variable.**

Logical Operations

➤ **AND:** $Z = X \times Y$ is read “Z is equal to X AND Y.”

$Z = 1$ if and only if $X = 1$ and $Y = 1$; otherwise $Z = 0$;

➤ **OR:** $Z = X + Y$ is read “Z is equal to X OR Y.”

$Z = 1$ if $X = 1$ or if $Y = 1$, or if both $X = 1$ and $Y = 1$;

$Z = 0$ if and only if $X = 0$ and $Y = 0$;

➤ **NOT:** $Z = \bar{X}$ is read “Z is equal to NOT X.”

If $X = 1$, $Z = 0$; but if $X = 0$, then $Z = 1$

Operator Definitions

- Operations are defined on the values "0" and "1" for each operator:

AND

$$0 \cdot 0 = 0$$

$$0 \cdot 1 = 0$$

$$1 \cdot 0 = 0$$

$$1 \cdot 1 = 1$$

OR

$$0 + 0 = 0$$

$$0 + 1 = 1$$

$$1 + 0 = 1$$

$$1 + 1 = 1$$

NOT

$$\overline{0} = 1$$

$$\overline{1} = 0$$

- **Note:** The statement:

$1 + 1 = 2$ (read “one plus one equals two”)

is not the same as

$1 + 1 = 1$ (read “1 or 1 equals 1”).

Truth Tables

- **Truth table** – a tabular listing of the values of a function for all possible combinations of values on its arguments
- **Example: Truth tables for the basic logic operations:**

AND		
X	Y	$Z = X \cdot Y$
0	0	0
0	1	0
1	0	0
1	1	1

OR		
X	Y	$Z = X + Y$
0	0	0
0	1	1
1	0	1
1	1	1

NOT	
X	$Z = \overline{X}$
0	1
1	0

Logic Function Implementation

➤ Using Switches

– For inputs:

- logic 1 is switch closed
- logic 0 is switch open


– For outputs:

- logic 1 is light on
- logic 0 is light off.


– NOT uses a switch such that:

- logic 1 is switch open
- logic 0 is switch closed


Switches in parallel => OR

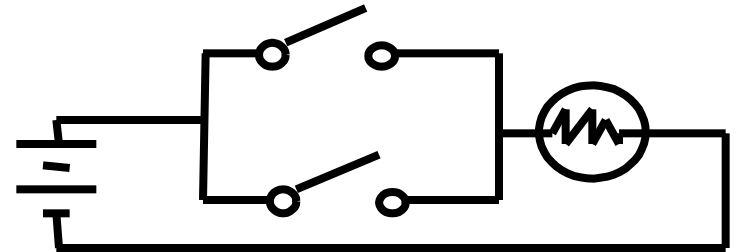

Switches in series => AND

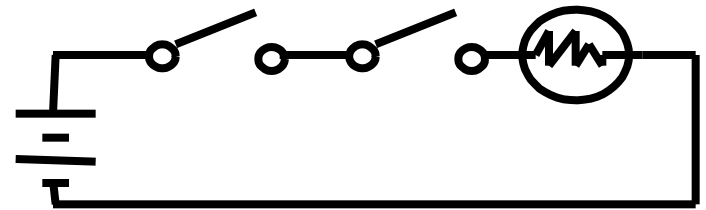


Normally-closed switch => NOT

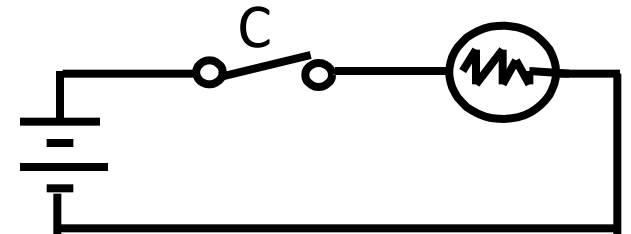

Logic Function Implementation (Continued)

➤ Example: Logic Using Switches

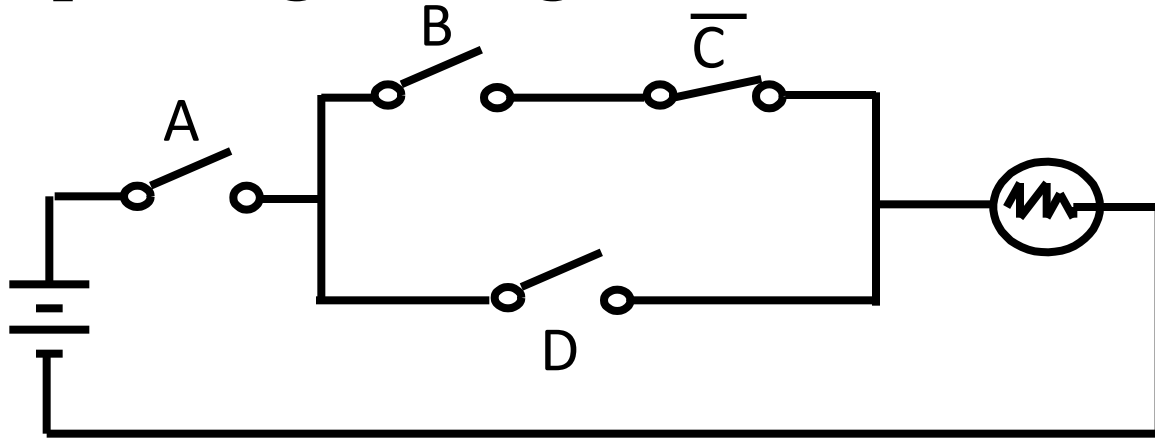

➤ Light is on ($L = 1$) for

$$L(A, B, C, D) = A ((B \overline{C}) + D) = A B \overline{C} + A D$$




and off ($L = 0$), otherwise.

Logic Gates

- In the earliest computers, switches were opened and closed by magnetic fields produced by energizing coils in *relays*. The switches in turn opened and closed the current paths.
- Later, *vacuum tubes* that open and close current paths electronically replaced relays.
- Today, *transistors* are used as electronic switches that open and close current paths.
- Optional: Chapter 6 – Part 1: The Design Space


Logic Gate Symbols and Behavior

➤ Logic gates have special symbols:

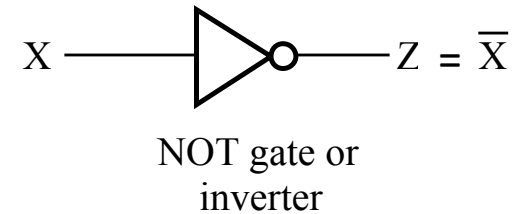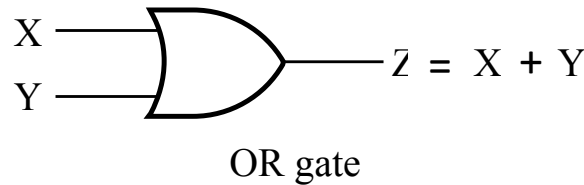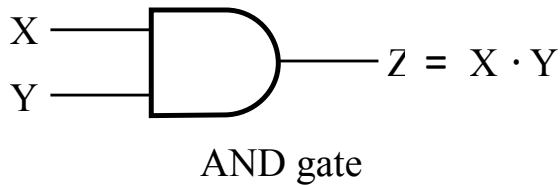

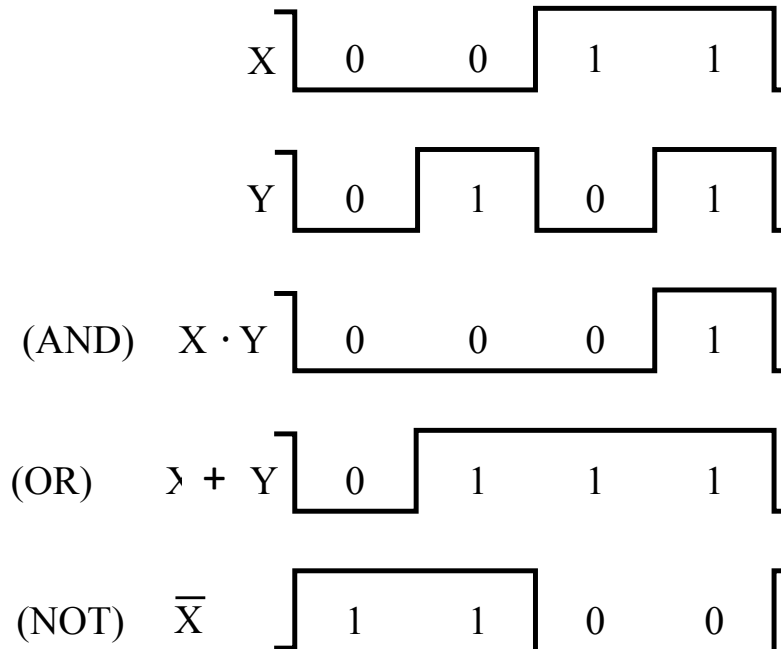(a) Graphic symbols


➤ And waveform behavior in time as follows:



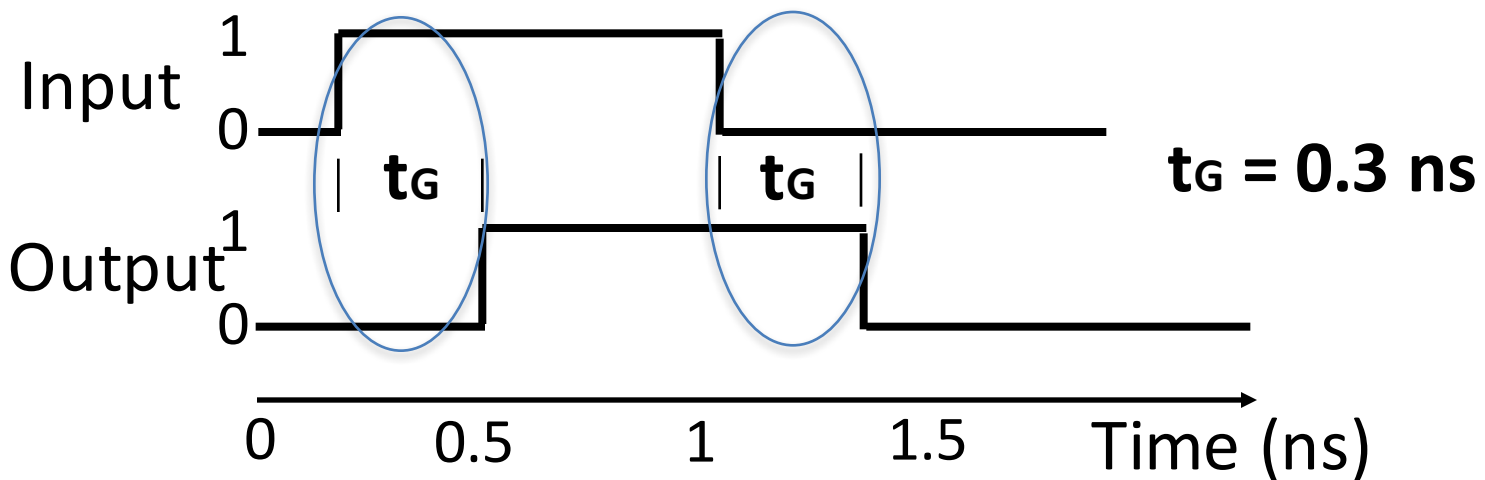(b) Timing diagram

Gate Delay

- In actual physical gates, if one or more input changes causes the output to change, the output change does not occur instantaneously.
- The delay between an input change(s) and the resulting output change is the *gate delay* denoted by t_G :





NOT AND (NAND)

True and False

A	B	L
F	F	T
T	F	T
F	T	T
T	T	F

1 and 0

A	B	L
0	0	1
1	0	1
0	1	1
1	1	0

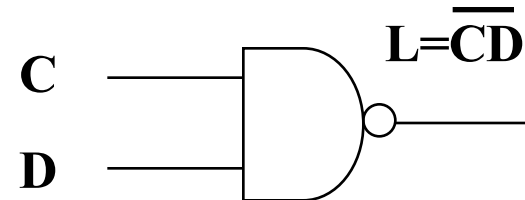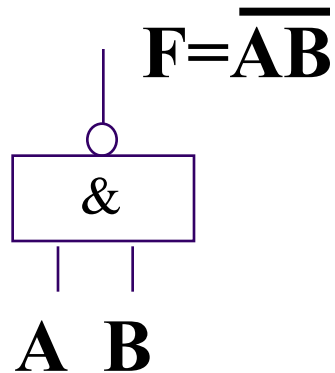


Graphic symbols

NOT OR (NOR)


True and False

<i>A</i>	<i>B</i>	<i>L</i>
F	F	T
T	F	F
F	T	F
T	T	F

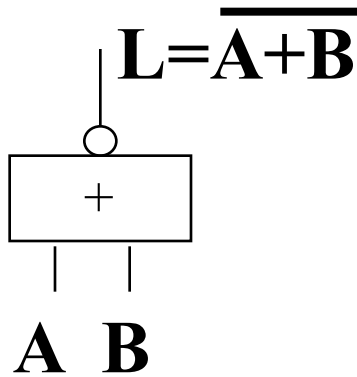

1 and 0

<i>A</i>	<i>B</i>	<i>L</i>
0	0	1
1	0	0
0	1	0
1	1	0

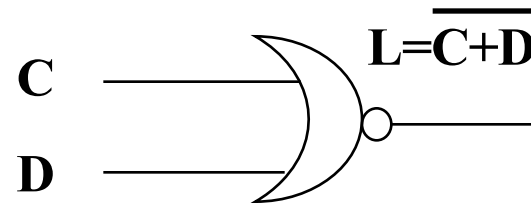


Graphic symbols

AND-OR-INVERT (AOI)

W X Y Z F

0	0	0	0	1
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
0	1	0	0	1
0	1	0	1	1
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

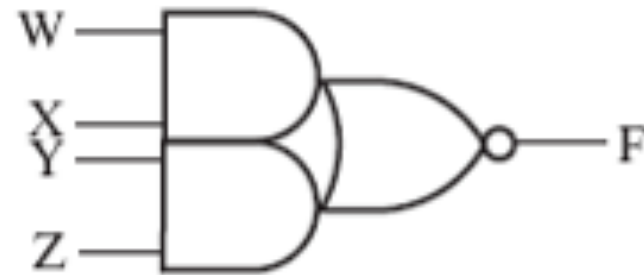

Graphic symbols



Exclusive-OR (XOR)

True and False

A	B	L
F	F	F
T	F	T
F	T	T
T	T	F

1 and 0

A	B	L
0	0	0
1	0	1
0	1	1
1	1	0

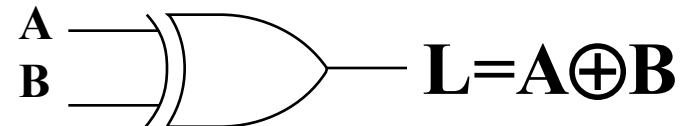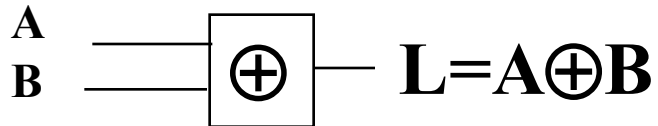

Graphic symbols

Eight Identities of XOR

$$X \oplus 0 = X$$

$$X \oplus 1 = \overline{X}$$

$$X \oplus X = 0$$

$$X \oplus \overline{X} = 1$$

$$X \oplus \overline{Y} = \overline{X \oplus Y}$$

$$\overline{X} \oplus Y = \overline{X \oplus Y}$$

$$X \oplus Y = Y \oplus X$$

$$(X \oplus Y) \oplus Z = X \oplus (Y \oplus Z) = X \oplus Y \oplus Z$$

$$X \oplus Y = X\overline{Y} + \overline{X}Y$$




Exclusive-NOR (XNOR)

True and False

<i>A</i>	<i>B</i>	<i>L</i>
F	F	T
T	F	F
F	T	F
T	T	T

1 and 0


<i>A</i>	<i>B</i>	<i>L</i>
0	0	1
1	0	0
0	1	0
1	1	1

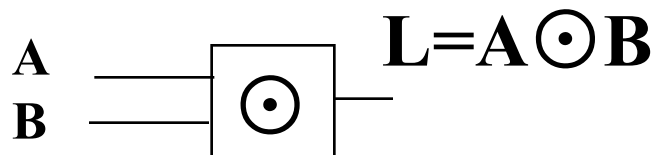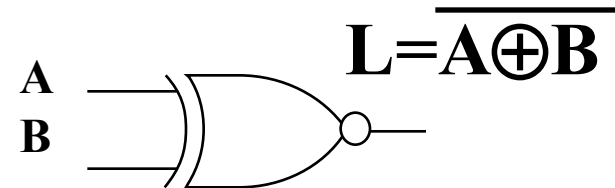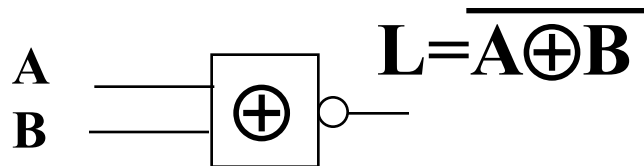


Graphic symbols

Multiple-input gates

OR:

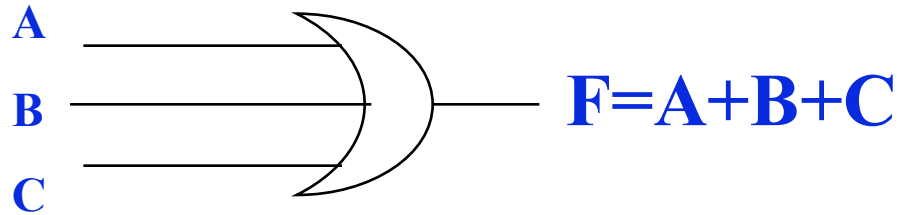

AND:

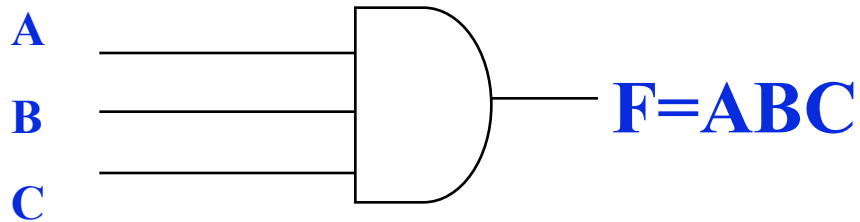

Boolean Algebra

- deals with binary variables and logic operations (AND, OR, NOT etc.).
- A Boolean expression is an algebraic expression formed by (**Example: $(A + C) \cdot B + 0$**)
 - binary variables
 - Constants 1 or 0
 - Logic operation symbols
- A Boolean function is a Boolean equation consisting of **Example: $F = (A + C) \cdot B + 0$ or $F(A, B, C) = (A + C) \cdot B + 0$**
 - a binary variables
 - a “=”
 - a Boolean expression

Boolean Function/Equation


Truth Table

X Y Z	F = X + \overline{Y} Z
0 0 0	0
0 0 1	1
0 1 0	0
0 1 1	0
1 0 0	1
1 0 1	1
1 1 0	1
1 1 1	1

Equation

$$F = X + \overline{Y} Z$$

Logic Diagram

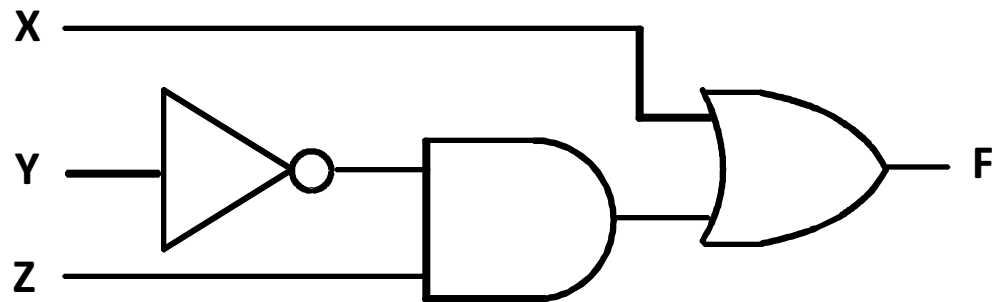

- The output of Boolean functions can be single or multiple.
- Boolean equations, truth tables and logic diagrams describe the same function!
- Truth tables are unique; expressions and logic diagrams are not. This gives flexibility in implementing functions.

Boolean Operator Precedence

- **The order of evaluation in a Boolean expression is:**
 1. Parentheses
 2. NOT
 3. AND
 4. OR
- **Consequence: Parentheses appear around OR expressions**
- **Example: $F = A(B + C)(\overline{C} + D)$**

Boolean Algebra

➤ An algebraic structure defined on a set of at least two elements, together with three binary operators (denoted $+$, \cdot and $\overline{}$) that satisfies the following basic identities:

1. $X + 0 = X$

2. $X \cdot 1 = X$

3. $X + 1 = 1$

4. $X \cdot 0 = 0$

5. $X + X = X$

6. $X \cdot X = X$

7. $X + \overline{X} = 1$

8. $X \cdot \overline{X} = 0$

9. $\overline{\overline{X}} = X$

10. $X + Y = Y + X$

11. $XY = YX$

Commutative

12. $(X + Y) + Z = X + (Y + Z)$

13. $(XY)Z = X(YZ)$

Associative

14. $X(Y + Z) = XY + XZ$

15. $X + YZ = (X + Y)(X + Z)$

Distributive

16. $\overline{X + Y} = \overline{X} \cdot \overline{Y}$

17. $\overline{X \cdot Y} = \overline{X} + \overline{Y}$

DeMorgan's

Property of **Duality** of Boolean algebra

- The dual of an algebraic expression is obtained by interchanging $+$ and \cdot , and replacing 0s by 1s and 1 by 0.

$$\text{Example: } F = (A + C) \cdot B + 0$$

$$\text{dual } F = (A \cdot C + B) \cdot 1 = A \cdot C + B$$

$$\text{Example: } G = X \cdot Y + (\overline{W + Z})$$

$$\text{dual } G = ((X+Y) \cdot (\overline{W \cdot Z})) = ((X+Y) \cdot (W + Z))$$

- Note the order of evaluation, add $()$ if necessary
- If F is the dual of G , then G is also the dual of F
- If $F=G$, then their duals are also equal.

Property of **Duality** of Boolean algebra

- Unless it happens to be self-dual, the dual of an expression does not equal the expression itself.
- Self-dual

Example: $H = A \cdot B + A \cdot C + B \cdot C$

$$\text{dual } H = (A + B)(A + C)(B + C)$$

$$= (A + BC)(B + C) = AB + AC + BC.$$

So H is self-dual !

Complementing Functions

➤ Use DeMorgan's Theorem to complement a function:

1. Interchange AND and OR operators

2. Complement each constant value and literal

➤ Example: Complement $F = \bar{X}Y\bar{Z} + X\bar{Y}\bar{Z}$

$$\bar{F} = (X + \bar{Y} + Z)(\bar{X} + Y + Z)$$

➤ Example: Complement $G = (\bar{a} + bc)\bar{d} + e$

$$\bar{G} = ((a(\bar{b} + \bar{c})) + d)\bar{e} = (a(\bar{b} + \bar{c}) + d)\bar{e}$$

➤ Difference between it and Dual?

– Without complementing variable in dual

Other Useful Theorems

➤ $x \times y + \bar{x} \times y = y$ $(x + y)(\bar{x} + y) = y$ **Minimization**

➤ $x + x \cdot y = x$ $x \cdot (x + y) = x$ **Absorption**

➤ $x + \bar{x} \times y = x + y$ $x \times (\bar{x} + y) = x \times y$ **Simplification**

➤ $x \times y + \bar{x} \times z + y \times z = x \times y + \bar{x} \times z$ **Consensus**

$$(x + y) \times (\bar{x} + z) \times (y + z) = (x + y) \times (\bar{x} + z)$$

➤ $\overline{x + y} = \bar{x} \times \bar{y}$ $\overline{x \times y} = \bar{x} + \bar{y}$ **DeMorgan's Laws**

Proof of Absorption Theorem

➤ $A + A \cdot B = A$ (Absorption Theorem)

Proof Steps	Justification (identity or theorem)
-------------	-------------------------------------

$A + A \cdot B$	
-----------------	--

$= A \cdot 1 + A \cdot B$	$X = X \cdot 1$
---------------------------	-----------------

$= A \cdot (1 + B)$	$X \cdot Y + X \cdot Z = X \cdot (Y + Z)$ (Distributive Law)
---------------------	--

$= A \cdot 1$	$1 + X = 1$
---------------	-------------

$= A$	$X \cdot 1 = X$
-------	-----------------

➤ Compute the dual on both sides, the equation is equal either

$$A \cdot (A+B) = A$$

Proof of Minimization Theorem

➤ $AB + \overline{A}\overline{B} = A$ (Minimization Theorem)

Proof Steps	Justification (identity or theorem)
-------------	-------------------------------------

$AB + \overline{A}\overline{B}$	
---------------------------------	--

$= A(B + \overline{B})$	$X \cdot Y + X \cdot Z = X \cdot (Y + Z)$ (Distributive Law)
-------------------------	--

$= A \cdot 1$	$1 + X = 1$
---------------	-------------

$= A$	
-------	--

➤ Compute the dual on both sides, the equation is equal either

$$(A+B) \cdot (\overline{A+B}) = A$$

Proof of Simplification Theorem

➤ $A + \overline{A}B = A + B$ (Simplification Theorem)

Proof Steps	Justification (identity or theorem)
--------------------	--

$$A + \overline{A}B$$

$$= (A + \overline{A})(A + B) \quad X + Y \cdot Z = (X+Y) \cdot (X + Z) \text{ (Distributive Law)}$$

$$= 1 \cdot (A+B) \quad X + X = 1$$

$$= A + B$$

➤ Compute the dual on both sides, the equation is equal either

$$A(\overline{A+B}) = \overline{AB}$$

Proof of Consensus Theorem

➤ $AB + \overline{A}C + BC = AB + \overline{A}C$ (Consensus Theorem)

Proof Steps **Justification (identity or theorem)**

$$AB + \overline{A}C + BC$$

$$= AB + \overline{A}C + 1 \cdot BC \quad ? \quad 1 \cdot X = X$$

$$= AB + \overline{A}C + (A + \overline{A}) \cdot BC \quad ? \quad X + X' = 1$$

$$= AB + A'C + ABC + A'BC \quad X(Y + Z) = XY + XZ \text{ (Distributive Law)}$$

$$= AB + ABC + A'C + A'BC \quad X + Y = Y + X \text{ (Commutative Law)}$$

$$= AB \cdot 1 + ABC + A'C \cdot 1 + A'C \cdot B$$

$$X \cdot 1 = X, X \cdot Y = Y \cdot X \text{ (Commutative Law)}$$

$$= AB(1 + C) + A'C(1 + B) \quad X(Y + Z) = XY + XZ \text{ (Distributive Law)}$$

$$= AB \cdot 1 + A'C \cdot 1 = AB + A'C \quad X \cdot 1 = X$$

Proof of the 15th basic identity

➤ Using the absorption theorem

$$X + XY = X$$

➤ $X + YZ = (X+Y)(X+Z)$

– From the right side

$$(X+Y)(X+Z) = X+XY+XZ+YZ$$

$$= X + XZ + YZ$$

$$= X + YZ$$

Proof of DeMorgan's Laws

$$\overline{x + y} = \bar{x} \times \bar{y}$$

$$\overline{x \times y} = \bar{x} + \bar{y}$$

To show this we need to show that $A + B = 1$ and $A \cdot B = 0$ with $A = x + y$ and $B = x' \cdot y'$. This proves that $x' \cdot y' = (x + y)'$.

Part 1: Show $x + y + x' \cdot y' = 1$.

$$x + y + x' \cdot y'$$

$$= (x + y + x') (x + y + y')$$

$$= (x + x' + y) (x + y + y')$$

$$= (1 + y)(x + 1)$$

$$= 1 \cdot 1$$

$$= 1$$

$$X + YZ = (X + Y)(X + Z) \text{ (Distributive Law)}$$

$$X + Y = Y + X \text{ (Commutative Law)}$$

$$X + X' = 1$$

$$1 + X = 1$$

$$1 \cdot X = 1$$

Proof of DeMorgan's Laws

$$\overline{x + y} = \bar{x} \times \bar{y}$$

$$\overline{x \times y} = \bar{x} + \bar{y}$$

To show this we need to show that $A + A' = 1$ and $A \cdot A' = 0$ with $A = x + y$ and $A' = x' \cdot y'$. This proves that $x' \cdot y' = (x + y)'$.

Part 2: Show $(x + y) \cdot x' \cdot y' = 0$.

$$\begin{aligned} & (x + y) \cdot x' \cdot y' \\ &= (x \cdot x' \cdot y' + y \cdot x' \cdot y') && X(Y + Z) = XY + XZ \text{ (Distributive Law)} \\ &= (x \cdot x' \cdot y' + y \cdot y' \cdot x') && XY = YX \text{ (Commutative Law)} \\ &= (0 \cdot y' + 0 \cdot x') && X \cdot X' = 0 \\ &= (0 + 0) && 0 \cdot X = 0 \\ &= 0 && X + 0 = X \text{ (With } X = 0) \end{aligned}$$

Based on the above two parts, $x' \cdot y' = (x + y)'$

The second one is proved by duality.

Example: Boolean Algebraic Proofs

➤ $(\overline{X + Y})Z + X\overline{Y} = \overline{Y}(X + Z)$

Proof Steps **Justification (identity or theorem)**

$$(\overline{X + Y})Z + X\overline{Y}$$

$$= X' Y' Z + X Y'$$

$$(A + B)' = A' \cdot B' \text{ (DeMorgan's Law)}$$

$$= Y' X' Z + Y' X$$

$$A \cdot B = B \cdot A \text{ (Commutative Law)}$$

$$= Y' (X' Z + X)$$

$$A(B + C) = AB + AC \text{ (Distributive Law)}$$

$$= Y' (X' + X)(Z + X)$$

$$A + BC = (A + B)(A + C) \text{ (Distributive Law)}$$

$$= Y' \cdot 1 \cdot (Z + X)$$

$$A + A' = 1$$

$$= Y' (X + Z)$$

$$1 \cdot A = A, A + B = B + A \text{ (Commutative Law)}$$

Expression Simplification

- Target: the smallest number of literals and the smallest number of terms (complemented and uncomplemented variables):
- AND-OR forms

$$\begin{aligned} & A B + \bar{A} C D + \bar{A} B D + \bar{A} C \bar{D} + A B C D \\ = & AB + ABCD + \bar{A} C D + \bar{A} C \bar{D} + \bar{A} B D \\ = & AB + AB(CD) + \bar{A} C (D + \bar{D}) + \bar{A} B D \\ = & AB + \bar{A} C + \bar{A} B D = B(A + \bar{A}D) + \bar{A}C \\ = & B (A + D) + \bar{A} C \quad 5 \text{ literals} \end{aligned}$$

Expression Simplification

➤ OR-AND forms

$$F = (\bar{A} + \bar{B})(\bar{A} + \bar{C} + D)(A + C)(B + \bar{C})$$

➤ Dual

$$\begin{aligned} F' &= \bar{A}\bar{B} + \bar{A}\bar{C}D + AC + B\bar{C} \\ &= (\bar{A}\bar{B} + B\bar{C} + \bar{A}\bar{C}D) + AC \\ &= \bar{A}\bar{B} + B\bar{C} + AC \end{aligned}$$

➤ Dual of $F' \Rightarrow F$

$$F = F'' = (\bar{A} + \bar{B})(B + \bar{C})(A + C)$$

Example: Simplify Expression

$$L = AB + \overline{A}\overline{C} + \overline{B}C + \overline{C}B + \overline{B}D + \overline{D}B + ADE(F + G)$$

$$L = \overline{\overline{A}\overline{B}\overline{C}} + \overline{B}C + \overline{C}B + \overline{B}D + \overline{D}B + ADE(F + G) \quad \text{DeMorgan Laws}$$

$$= A + \overline{B}C + \overline{C}B + \overline{B}D + \overline{D}B + ADE(F + G) \quad A + \overline{A}B = A + B$$

$$= A + \overline{B}C + \overline{C}B + \overline{B}D + \overline{D}B \quad A + AB = A$$

$$= A + \overline{B}C(D + \overline{D}) + \overline{C}B + \overline{B}D + \overline{D}B(C + \overline{C}) \quad A + \overline{A} = 1$$

$$= A + \overline{B}CD + \overline{B}C\overline{D} + \overline{C}B + \overline{B}D + \overline{D}BC + \overline{D}B\overline{C} \quad \text{Distributive Laws}$$

$$= A + \overline{B}C\overline{D} + \overline{C}B + \overline{B}D + \overline{D}BC \quad A + AB = A$$


$$= A + C\overline{D}(\overline{B} + B) + \overline{C}B + \overline{B}D$$

$$= A + C\overline{D} + \overline{C}B + \overline{B}D \quad A + \overline{A} = 1$$

Sum of Products, Products of Sum


➤ Sum of products

$$F = \bar{Y} + \bar{X}Y\bar{Z} + XY$$

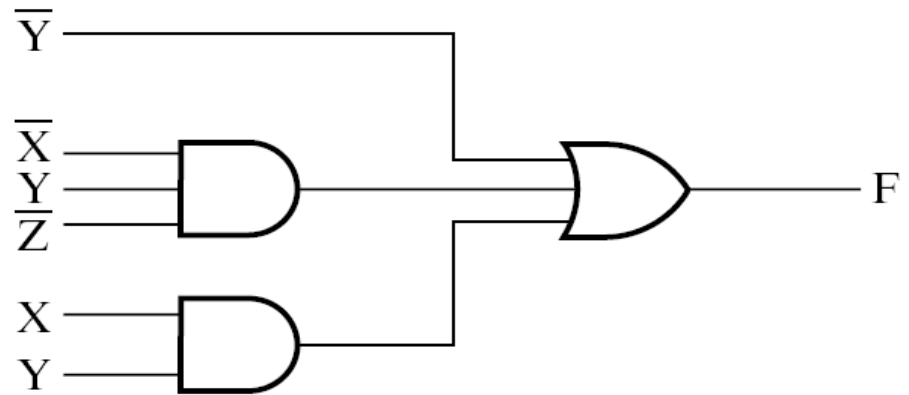

➤ Product of sums

$$F = X(\bar{Y} + Z)(X + Y + \bar{Z})$$

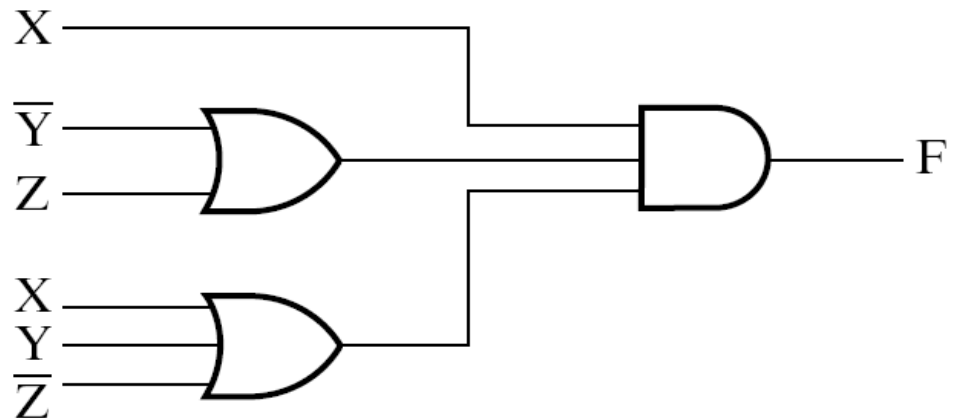

Overview – Canonical Forms

- **What are Canonical Forms?**
- **Minterms and Maxterms**
- **Index Representation of Minterms and Maxterms**
- **Sum-of-Minterm (SOM) Representations**
- **Product-of-Maxterm (POM) Representations**
- **Representation of Complements of Functions**
- **Conversions between Representations**

Canonical Forms

- **It is useful to specify Boolean functions in a form that:**
 - **Allows comparison for equality.**
 - **Has a correspondence to the truth tables**
- **Canonical Forms in common usage:**
 - **Sum of Minterms (SOM)**
 - **Product of Maxterms (POM)**
 - **Any function can be expressed to the canonical form**

Minterms

- Minterms are **AND** terms with every variable present in either true or complemented form.
- Given that each binary variable may appear normal (e.g., x) or complemented (e.g., \overline{x}), there are 2^n minterms for n variables.

X	Y	Z	Product Term	Symbol	m_0	m_1	m_2	m_3	m_4	m_5	m_6	m_7
0	0	0	$\overline{X}\overline{Y}\overline{Z}$	m_0	1	0	0	0	0	0	0	0
0	0	1	$\overline{X}\overline{Y}Z$	m_1	0	1	0	0	0	0	0	0
0	1	0	$\overline{X}Y\overline{Z}$	m_2	0	0	1	0	0	0	0	0
0	1	1	$\overline{X}YZ$	m_3	0	0	0	1	0	0	0	0
1	0	0	$X\overline{Y}\overline{Z}$	m_4	0	0	0	0	1	0	0	0
1	0	1	$X\overline{Y}Z$	m_5	0	0	0	0	0	1	0	0
1	1	0	$XY\overline{Z}$	m_6	0	0	0	0	0	0	1	0
1	1	1	XYZ	m_7	0	0	0	0	0	0	0	1

Minterms

- **Complemented or uncomplemented? A literal is**
 - complemented if the corresponding bit is 0
 - Uncomplemented if the corresponding bit is 1
- **The index:** the decimal equivalent of the binary combination corresponding to the Minterm

X	Y	Z	Product Term	Symbol	m ₀	m ₁	m ₂	m ₃	m ₄	m ₅	m ₆	m ₇
0	0	0	$\overline{X}\overline{Y}\overline{Z}$	m ₀	1	0	0	0	0	0	0	0
0	0	1	$\overline{X}\overline{Y}Z$	m ₁	0	1	0	0	0	0	0	0
0	1	0	$\overline{X}Y\overline{Z}$	m ₂	0	0	1	0	0	0	0	0
0	1	1	$\overline{X}YZ$	m ₃	0	0	0	1	0	0	0	0
1	0	0	$X\overline{Y}\overline{Z}$	m ₄	0	0	0	0	1	0	0	0
1	0	1	$X\overline{Y}Z$	m ₅	0	0	0	0	0	1	0	0
1	1	0	$XY\overline{Z}$	m ₆	0	0	0	0	0	0	1	0
1	1	1	XYZ	m ₇	0	0	0	0	0	0	0	1

Maxterms

- Maxterms are OR terms with every variable in true or complemented form.
- Given that each binary variable may appear normal (e.g., x) or complemented (e.g., \bar{x}), there are 2^n maxterms for n variables.

X	Y	Z	Sum Term	Symbol	M_0	M_1	M_2	M_3	M_4	M_5	M_6	M_7
0	0	0	$X+Y+Z$	M_0	0	1	1	1	1	1	1	1
0	0	1	$X+Y+\bar{Z}$	M_1	1	0	1	1	1	1	1	1
0	1	0	$X+\bar{Y}+Z$	M_2	1	1	0	1	1	1	1	1
0	1	1	$X+\bar{Y}+\bar{Z}$	M_3	1	1	1	0	1	1	1	1
1	0	0	$\bar{X}+Y+Z$	M_4	1	1	1	1	0	1	1	1
1	0	1	$\bar{X}+Y+\bar{Z}$	M_5	1	1	1	1	1	0	1	1
1	1	0	$\bar{X}+\bar{Y}+Z$	M_6	1	1	1	1	1	1	0	1
1	1	1	$\bar{X}+\bar{Y}+\bar{Z}$	M_7	1	1	1	1	1	1	1	0

Maxterms

- **Complemented or uncomplemented? A literal is**
 - complemented if the corresponding bit is **1**
 - Uncomplemented if the corresponding bit is **0**
- **The index:** the decimal equivalent of the binary combination corresponding to the Minterm

X	Y	Z	Sum Term	Symbol	M ₀	M ₁	M ₂	M ₃	M ₄	M ₅	M ₆	M ₇
0	0	0	$X+Y+Z$	M ₀	0	1	1	1	1	1	1	1
0	0	1	$X+Y+\bar{Z}$	M ₁	1	0	1	1	1	1	1	1
0	1	0	$X+\bar{Y}+Z$	M ₂	1	1	0	1	1	1	1	1
0	1	1	$X+\bar{Y}+\bar{Z}$	M ₃	1	1	1	0	1	1	1	1
1	0	0	$\bar{X}+Y+Z$	M ₄	1	1	1	1	0	1	1	1
1	0	1	$\bar{X}+Y+\bar{Z}$	M ₅	1	1	1	1	1	0	1	1
1	1	0	$\bar{X}+\bar{Y}+Z$	M ₆	1	1	1	1	1	1	0	1
1	1	1	$\bar{X}+\bar{Y}+\bar{Z}$	M ₇	1	1	1	1	1	1	1	0

Minterm and Maxterm Relationship

➤ Review: DeMorgan's Theorem

$$\overline{x \cdot y} = \bar{x} + \bar{y} \text{ and } \overline{x + y} = \bar{x} \times \bar{y}$$

➤ Two-variable example:

$$M_2 = \bar{x} + y \text{ and } m_2 = x \cdot \bar{y}$$

Thus M_2 is the complement of m_2 and vice-versa.

➤ Since DeMorgan's Theorem holds for n variables, the above holds for terms of n variables

➤ giving:

$$M_i = \overline{m_i} \text{ and } m_i = \overline{M_i}$$

Thus M_i is the complement of m_i .

Index	Minterm	Maxterm
0	$\bar{x} \bar{y}$	$x + y$
1	$\bar{x} y$	$x + \bar{y}$
2	$x \bar{y}$	$\bar{x} + y$
3	$x y$	$\bar{x} + \bar{y}$

Observations

- In the function tables:
 - Each minterm has one and only one 1 present in the 2^n terms (a minimum of 1s). All other entries are 0.
 - Each maxterm has one and only one 0 present in the 2^n terms. All other entries are 1 (a maximum of 1s).
- We can implement any function by "ORing" the minterms corresponding to "1" entries in the function table. These are called the minterms of the function.
- We can implement any function by "ANDing" the maxterms corresponding to "0" entries in the function table. These are called the maxterms of the function.
- This gives us two canonical forms:
 - Sum of Minterms (SOM)
 - Product of Maxterms (POM)for stating any Boolean function.

Sum of Minterms (SOM)

➤ **Example:** Find $F_1 = m_1 + m_4 + m_7$

➤ $F_1 = \bar{x} \bar{y} z + x \bar{y} \bar{z} + x y z$

x y z	index	m1	+	m4	+	m7	= F1
0 0 0	0	0	+	0	+	0	= 0
0 0 1	1	1	+	0	+	0	= 1
0 1 0	2	0	+	0	+	0	= 0
0 1 1	3	0	+	0	+	0	= 0
1 0 0	4	0	+	1	+	0	= 1
1 0 1	5	0	+	0	+	0	= 0
1 1 0	6	0	+	0	+	0	= 0
1 1 1	7	0	+	0	+	1	= 1

Product of Maxterms (POM)

➤ Example: Implement F1 in maxterms:

$$F_1 = M_0 \cdot M_2 \cdot M_3 \cdot M_5 \cdot M_6$$

$$F_1 = (x + y + z) \cdot (x + \bar{y} + z) \cdot (x + \bar{y} + \bar{z}) \cdot (\bar{x} + y + \bar{z}) \cdot (\bar{x} + \bar{y} + z)$$

x y z	i	$M_0 \cdot M_2 \cdot M_3 \cdot M_5 \cdot M_6 = F_1$
0 0 0	0	$0 \cdot 1 \cdot 1 \cdot 1 \cdot 1 = 0$
0 0 1	1	$1 \cdot 1 \cdot 1 \cdot 1 \cdot 1 = 1$
0 1 0	2	$1 \cdot 0 \cdot 1 \cdot 1 \cdot 1 = 0$
0 1 1	3	$1 \cdot 1 \cdot 0 \cdot 1 \cdot 1 = 0$
1 0 0	4	$1 \cdot 1 \cdot 1 \cdot 1 \cdot 1 = 1$
1 0 1	5	$1 \cdot 1 \cdot 1 \cdot 0 \cdot 1 = 0$
1 1 0	6	$1 \cdot 1 \cdot 1 \cdot 1 \cdot 0 = 0$
1 1 1	7	$1 \cdot 1 \cdot 1 \cdot 1 \cdot 1 = 1$

Canonical Sum of Minterms

- Any Boolean function can be expressed as a Sum of Minterms.
 - For the function table, the minterms used are the terms corresponding to the 1's
 - For expressions, expand all terms first to explicitly list all minterms. Do this by “ANDing” any term missing a variable v with a term $(v + \bar{v})$.
- Example: Implement $f = x + \bar{x} \bar{y}$ as a sum of minterms.

First expand terms: $f = x(y + \bar{y}) + \bar{x} \bar{y}$

Then distribute terms: $f = xy + x\bar{y} + \bar{x} \bar{y}$

Express as sum of minterms: $f = m_3 + m_2 + m_0 = \Sigma_m(0, 2, 3)$

Canonical Product of Maxterms

- Any Boolean Function can be expressed as a Product of Maxterms (POM).
 - For the function table, the maxterms used are the terms corresponding to the 0's.
 - For an expression, expand all terms first to explicitly list all maxterms. Do this by first applying the second distributive law, “ORing” terms missing variable v with a term equal to $v \times \bar{v}$ and then applying the distributive law again.

- Example: Convert to product of maxterms:

$$f(x, y, z) = x + \bar{x} \bar{y}$$

Apply the distributive law:

$$x + \bar{x} \bar{y} = (x + \bar{x})(x + \bar{y}) = 1 \times (x + \bar{y}) = x + \bar{y}$$

Add missing variable z :

$$x + \bar{y} + z \times \bar{z} = (x + \bar{y} + z)(x + \bar{y} + \bar{z})$$

$$\text{Express as POM: } f = M_2 \cdot M_3 = \Pi_M(2, 3)$$

Function Complements

- The complement of a function expressed as a sum of minterms is constructed by selecting the minterms missing in the sum-of-minterms canonical forms.
- Alternatively, the complement of a function expressed by a Sum of Minterms form is simply the Product of Maxterms with the same indices.
- Example: Given $F(x, y, z) = \Sigma_m(1, 3, 5, 7)$
 $\bar{F}(x, y, z) = \Sigma_m(0, 2, 4, 6)$
 $\bar{F}(x, y, z) = \Pi_M(1, 3, 5, 7)$

Standard Forms

- Standard Sum-of-Products (SOP) form: equations are written as an OR of AND terms
- Standard Product-of-Sums (POS) form: equations are written as an AND of OR terms
- Examples:
 - SOP: $A B C + \bar{A} \bar{B} C + B$
 - POS: $(A + B) \cdot (A + \bar{B} + \bar{C}) \cdot C$
- These “mixed” forms are neither SOP nor POS
 - $(A B + C) (A + C)$
 - $A B \bar{C} + A C (A + B)$

Standard Sum-of-Products (SOP)

- **A sum of minterms form for n variables can be written down directly from a truth table.**
 - **Implementation of this form is a two-level network of gates such that:**
 - **The first level consists of n -input AND gates, and**
 - **The second level is a single OR gate (with fewer than 2^n inputs).**
- **This form often can be simplified so that the corresponding circuit is simpler.**

Standard Sum-of-Products (SOP)

➤ A Simplification Example:

➤ $F(A, B, C) = \Sigma m(1, 4, 5, 6, 7)$

➤ Writing the minterm expression:

$$F = \overline{A} \overline{B} C + A \overline{B} \overline{C} + A \overline{B} C + A B \overline{C} + A B C$$

➤ Simplifying:

$$F = A' B' C + A (B' C' + B C' + B' C + B C)$$

$$= A' B' C + A (B' + B) (C' + C)$$

$$= A' B' C + A \cdot 1 \cdot 1$$

$$= A' B' C + A$$

$$= B' C + A$$

➤ Simplified F contains 3 literals compared with 15 in minterm F

SOP and POS Observations

- **The previous examples show that:**
 - **Canonical Forms (Sum-of-minterms, Product-of-Maxterms), or other standard forms (SOP, POS) differ in complexity**
 - **Boolean algebra can be used to manipulate equations into simpler forms.**
 - **Simpler equations lead to simpler two-level implementations**
- **Questions:**
 - **How can we attain a “simplest” expression?**
 - **Is there only one minimum cost circuit?**
 - **The next part will deal with these issues.**

Home Assignment

2-1; 2-2a; 2-3a, c; 2-6b, d; 2-10a, c; 2-11a, b, d; 2-12b; 2-13a, c;