
Logic and Computer Design Fundamentals

Chapter 6 – Selected Design Topics

Part 2 Propagation Delay and Timing

Part 4 Programmable Implementation
Technologies

Yueming Wang (王跃明)

ymingwang@zju.edu.cn

2017

College of Computer Science, Zhejiang University

Qiushi Academy for Advanced Studies, Zhejiang University


Overview

- **Part 1 – The Design Space**
- **Part 2 – Propagation Delay and Timing**
 - **Propagation Delay**
 - **Delay Models**
 - **Cost/Performance Tradeoffs**
 - **Flip-Flop Timing**
 - **Circuit & System Level Timing**
- **Part 3 – Asynchronous Interactions**
- **Part 4 - Programmable Implementation Technologies**

Propagation Delay

- *Propagation delay* is the time for a change on an input of a gate to propagate to the output.
- Delay is usually measured at the 50% point with respect to the H and L output voltage levels.
- High-to-low (t_{PHL}) and low-to-high (t_{PLH}) output signal changes may have different propagation delays.
- High-to-low (HL) and low-to-high (LH) transitions are defined with respect to the output, not the input.
- An HL input transition causes:
 - an LH output transition if the gate inverts and
 - an HL output transition if the gate does not invert.


Propagation Delay (continued)

 

- Propagation delays measured at the midpoint between the L and H values

Propagation Delay Example

 
- Find t_{PHL} , t_{PLH} and t_{pd} for the signals given



Delay Models

- ***Transport delay*** - a change in the output in response to a change on the inputs occurs after a fixed specified delay
- ***Inertial delay*** - similar to transport delay, except that if the input changes such that the output is to change twice in a time interval less than the *rejection time*, the output changes do not occur. Models typical electronic circuit behavior, namely, rejects narrow “pulses” on the outputs




Delay Model Example

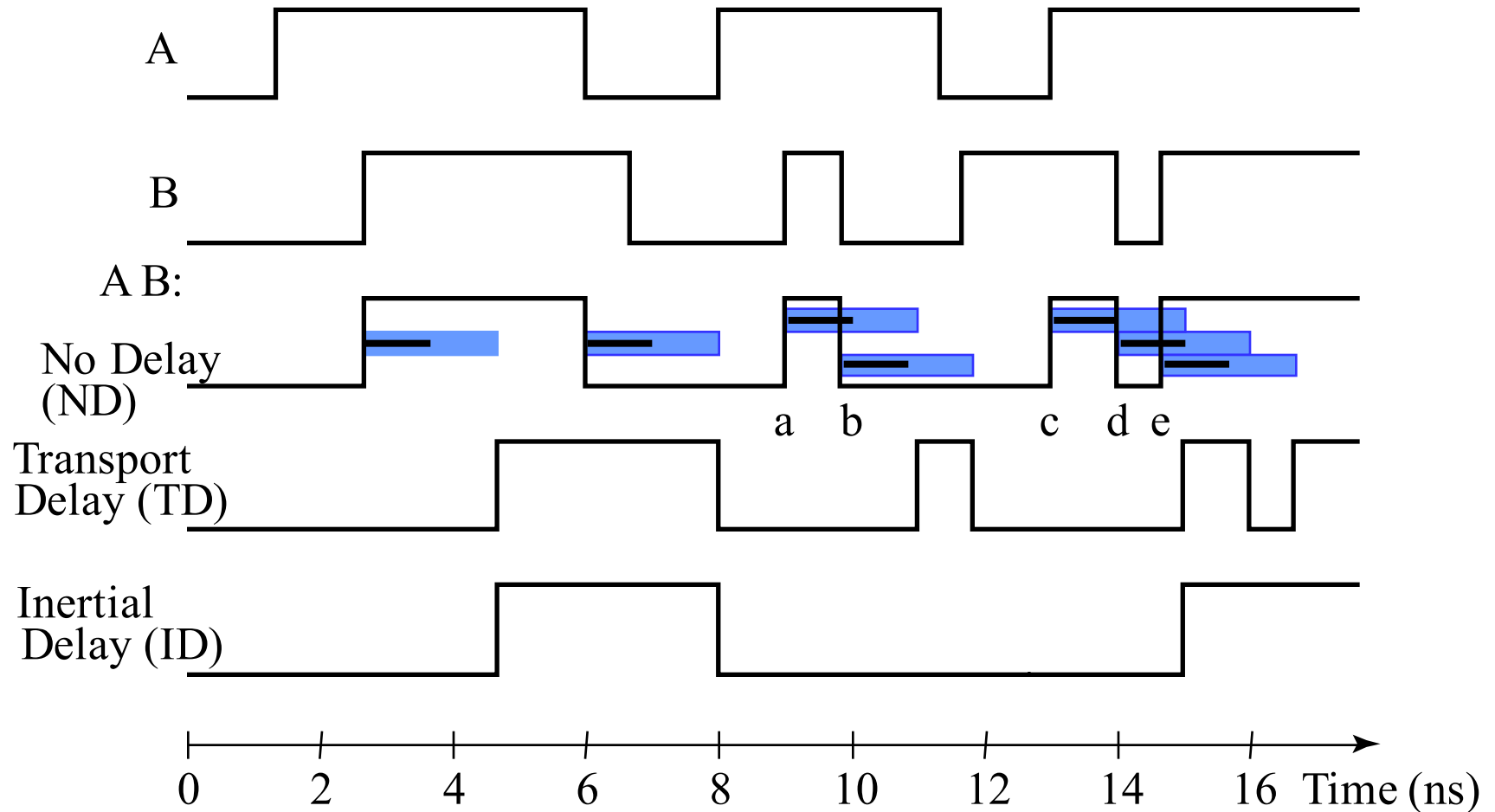

Propagation Delay = 2.0 ns Rejection Time = 1.0 ns

Circuit Delay

   - Suppose gates with delay n ns are represented for $n = 0.2$ ns, $n = 0.4$ ns, $n = 0.5$ ns, respectively:





Circuit Delay

- Consider a simple 2-input multiplexer:

- With function:

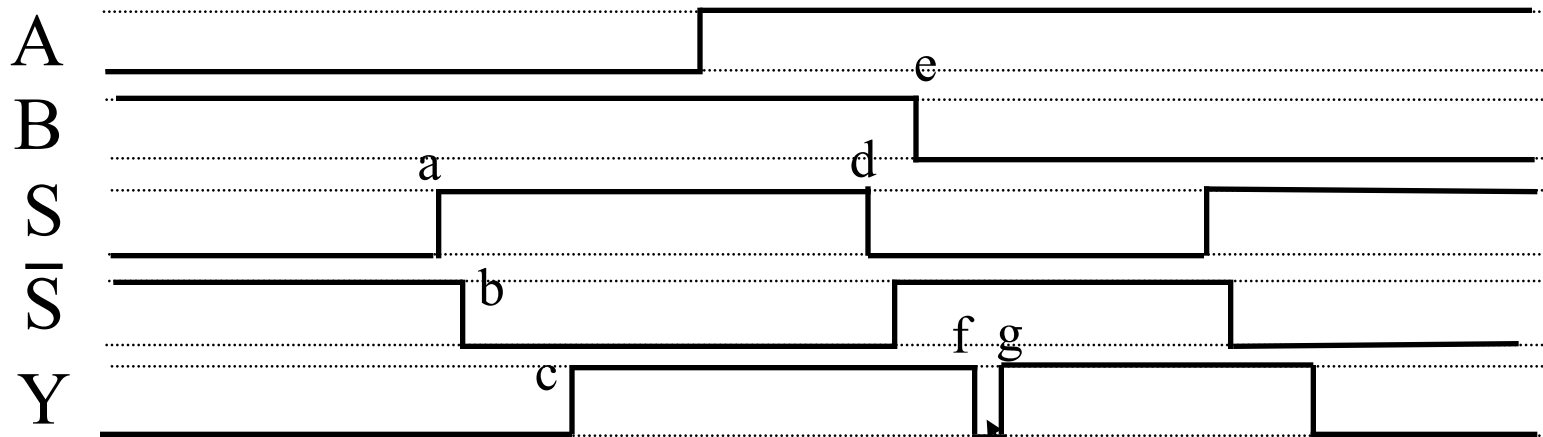 - $Y = A$ for $S = 0$
- $Y = B$ for $S = 1$



- “Glitch” is due to delay of inverter

Fan-out and Delay

- The fan-out loading a gate's output affects the gate's propagation delay
- Example:
 - One realistic equation for t_{pd} for a NAND gate with 4 inputs is:
$$t_{pd} = 0.07 + 0.021 SL \text{ ns}$$
 - SL is the number of standard loads the gate is driving, i. e., its fan-out in standard loads
 - For $SL = 4.5$, $t_{pd} = 0.165 \text{ ns}$
- If this effect is considered, the delay of a gate in a circuit takes on different values depending on the circuit load on its output.

Cost/Performance Tradeoffs

- **Gate-Level Example:**
 - **NAND gate G with 20 standard loads on its output has a delay of 0.45 ns and has a normalized cost of 2.0**
 - **A buffer H has a normalized cost of 1.5. The NAND gate driving the buffer with 20 standard loads gives a total delay of 0.33 ns**
 - **In which if the following cases should the buffer be added?**
 - 1. The cost of this portion of the circuit cannot be more than 2.5**
 - 2. The delay of this portion of the circuit cannot be more than 0.40 ns**
 - 3. The delay of this portion of the circuit must be less than 0.40 ns and the cost less than 3.0**
- **Tradeoffs can also be accomplished much higher in the design hierarchy**
- **Constraints on cost and performance have a major role in making tradeoffs**

Flip-Flop Timing Parameters

- t_s - setup time

- t_h - hold time


- t_w - clock pulse width

- t_{px} - propagation delay


- t_{PHL} - High-to-Low

- t_{PLH} - Low-to-High

- $t_{pd} - \max(t_{PHL}, t_{PLH})$

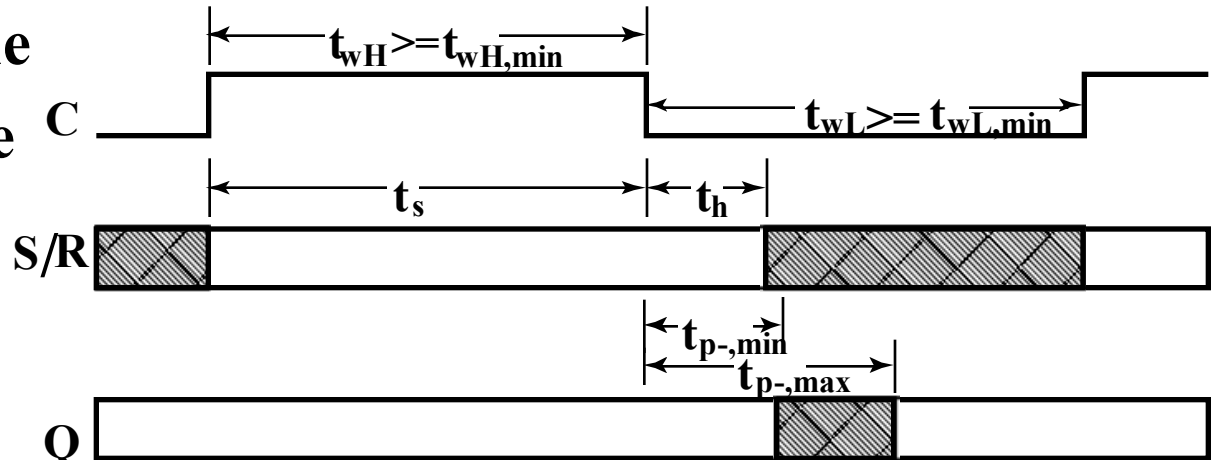

(a) Pulse-triggered (positive pulse)

 


(b) Edge-triggered (negative edge)

Flip-Flop Timing Parameters

- t_s - setup time
 - Master-slave - Equal to the width of the triggering pulse
 - Edge-triggered - Equal to a time interval that is generally much less than the width of the triggering pulse
- t_h - hold time - Often equal to zero
- t_{px} - propagation delay
 - Same parameters as for gates except
 - Measured from clock edge that triggers the output change to the output change

Circuit and System Level Timing

 - Consider a system comprised of ranks of flip-flops connected by logic:
- If the clock period is too short, some data changes will not propagate through the circuit to flip-flop inputs before the setup time interval begins




Circuit and System Level Timing

■ New Timing Components


- t_p - clock period - The interval between occurrences of a specific clock edge in a periodic clock
- $t_{pd,COMB}$ - total delay of combinational logic along the path from flip-flop output to flip-flop input
- t_{slack} - extra time in the clock period in addition to the sum of the delays and setup time on a path
 - Can be either positive or negative
 - Must be greater than or equal to zero on all paths for correct operation

Circuit and System Level Timing

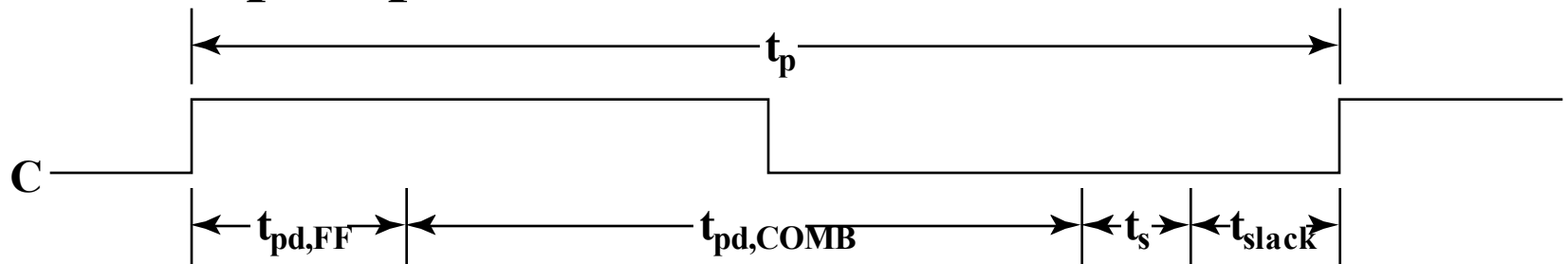- Timing components along a path from flip-flop to flip-flop



(a) Edge-triggered (positive edge)

 

(b) Pulse-triggered (negative pulse)

Circuit and System Level Timing

- **Timing Equations**

$$t_p = t_{\text{slack}} + (t_{\text{pd,FF}} + t_{\text{pd,COMB}} + t_s)$$

- For t_{slack} greater than or equal to zero,

$$t_p \geq \max (t_{\text{pd,FF}} + t_{\text{pd,COMB}} + t_s)$$

for all paths from flip-flop output to flip-flop input

- **Can be calculated more precisely by using t_{PHL} and t_{PLH} values instead of t_{pd} values, but requires consideration of inversions on paths**

Calculation of Allowable $t_{pd,COMB}$

- **Compare the allowable combinational delay for a specific circuit:**
 - a) Using edge-triggered flip-flops
 - b) Using master-slave flip-flops
- **Parameters**
 - $t_{pd,FF}(\max) = 1.0 \text{ ns}$
 - $t_s(\max) = 0.3 \text{ ns}$ for edge-triggered flip-flops
 - $t_s = t_{wH} = 1.0 \text{ ns}$ for master-slave flip-flops
 - Clock frequency = 250 MHz

Calculation of Allowable $t_{pd,COMB}$

- **Calculations: $t_p = 1/\text{clock frequency} = 4.0 \text{ ns}$**
 - **Edge-triggered: $4.0 \geq 1.0 + t_{pd,COMB} + 0.3$, $t_{pd,COMB} \leq 2.7 \text{ ns}$**
 - **Master-slave: $4.0 \geq 1.0 + t_{pd,COMB} + 1.0$, $t_{pd,COMB} \leq 2.0 \text{ ns}$**
- **Comparison: Suppose that for a gate, average $t_{pd} = 0.3 \text{ ns}$**
 - **Edge-triggered: Approximately 9 gates allowed on a path**
 - **Master-slave: Approximately 6 to 7 gates allowed on a path**

Overview

- **Part 1 – The Design Space**
- **Part 2 – Propagation Delay and Timing**
- **Part 3 – Asynchronous Interactions**
- **Part 4 - Programmable Implementation Technologies**
 - **Why Programmable Logic?**
 - **Programming Technologies**
 - **Read-Only Memories (ROMs)**
 - **Programmable Logic Arrays (PLAs)**
 - **Programmable Array Logic (PALs)**

Why Programmable Logic?

- **Facts:**
 - It is most economical to produce an IC in large volumes
 - Many designs required only small volumes of ICs
- **Need an IC that can be:**
 - Produced in large volumes
 - Handle many designs required in small volumes
- **A programmable logic part can be:**
 - made in large volumes
 - programmed to implement large numbers of different low-volume designs

Programmable Logic - More Advantages

- Many programmable logic devices are *field-programmable*, i. e., can be programmed outside of the manufacturing environment
- Most programmable logic devices are *erasable* and *reprogrammable*.
 - Allows “updating” a device or correction of errors
 - Allows reuse the device for a different design - the ultimate in re-usability!
 - Ideal for course laboratories
- Programmable logic devices can be used to prototype design that will be implemented for sale in regular ICs.
 - Complete Intel Pentium designs were actually prototyped with specialized systems based on large numbers of VLSI programmable devices!

Programming Technologies

- **Programming technologies are used to:**
 - **Control connections**
 - **Build lookup tables**
 - **Control transistor switching**
- **The technologies**
 - **Control connections**
 - **Mask programming**
 - **Fuse**
 - **Antifuse**
 - **Single-bit storage element**

Programming Technologies

- **The technologies (continued)**
 - **Build lookup tables**
 - **Storage elements (as in a memory)**
 - **Transistor Switching Control**
 - **Stored charge on a floating transistor gate**
 - **Erasable**
 - **Electrically erasable**
 - **Flash (as in Flash Memory)**
 - **Storage elements (as in a memory)**


Technology Characteristics

- **Permanent - Cannot be erased and reprogrammed**
 - Mask programming
 - Fuse
 - Antifuse
- **Reprogrammable**
 - **Volatile - Programming lost if chip power lost**
 - Single-bit storage element
 - **Non-Volatile**
 - Erasable
 - Electrically erasable
 - Flash (as in Flash Memory)


Programmable Configurations

- ***Read Only Memory (ROM)*** - a fixed array of AND gates and a programmable array of OR gates
- ***Programmable Array Logic (PAL)[®]*** - a programmable array of AND gates feeding a fixed array of OR gates.
- ***Programmable Logic Array (PLA)*** - a programmable array of AND gates feeding a programmable array of OR gates.
- ***Complex Programmable Logic Device (CPLD) /Field- Programmable Gate Array (FPGA)*** - complex enough to be called “architectures” - See VLSI Programmable Logic Devices reading supplement


ROM, PAL and PLA Configurations

 

(a) Programmable read-only memory (PROM)

 

 (b) Programmable array logic (PAL) device



(c) Programmable logic array (PLA) device

Read Only Memory

- **Read Only Memories (ROM) or Programmable Read Only Memories (PROM) have:**
 - **N input lines,**
 - **M output lines, and**
 - **2^N decoded minterms.**
- **Fixed AND array with 2^N outputs implementing all N-literal minterms.**
- **Programmable OR Array with M outputs lines to form up to M sum of minterm expressions.**

Read Only Memory


- A program for a ROM or PROM is simply a multiple-output truth table
 - If a 1 entry, a connection is made to the corresponding minterm for the corresponding output
 - If a 0, no connection is made
- Can be viewed as a *memory* with the inputs as *addresses* of *data* (output values), hence ROM or PROM names!

Read Only Memory Example

 - Example: A 8 X 4 ROM ($N = 3$ input lines, $M = 4$ output lines)

- The fixed "AND" array is a "decoder" with 3 inputs and 8 outputs implementing minterms.

- The programmable "OR" array uses a single line to represent all inputs to an OR gate. An "X" in the array corresponds to attaching the minterm to the OR



- Read Example: For input $(A_2, A_1, A_0) = 001$, output is $(F_3, F_2, F_1, F_0) = 0011$.
- What are functions F_3 , F_2 , F_1 and F_0 in terms of (A_2, A_1, A_0) ?

Example: Square of 3-bit input number


Inputs			Outputs						
A_2	A_1	A_0	B_5	B_4	B_3	B_2	B_1	B_0	Decimal
0	0	0	0	0	0	0	0	0	0
0	0	1	0	0	0	0	0	1	1
0	1	0	0	0	0	1	0	0	4
0	1	1	0	0	1	0	0	1	9
1	0	0	0	1	0	0	0	0	16
1	0	1	0	1	1	0	0	1	25
1	1	0	1	0	0	1	0	0	36
1	1	1	1	1	0	0	0	1	49

$$B_0 = A_0$$

$$B_1 = 0$$

 Example: Square of 3-bit input number

- **8 × 4 ROM are selected ROM Truth Table**



A ₂	A ₁	A ₀	B ₅	B ₄	B ₃	B ₂
0	0	0	0	0	0	0
0	0	1	0	0	0	0
0	1	0	0	0	0	1
0	1	1	0	0	1	0
1	0	0	0	1	0	0
1	0	1	0	1	1	0
1	1	0	1	0	0	1
1	1	1	1	1	0	0

Programmable Array Logic (PAL)

- The PAL is the opposite of the ROM, having a programmable set of ANDs combined with fixed ORs.
- Advantages
 - For given internal complexity, a PAL can have larger N and M
 - Some PALs have outputs that can be complemented, adding POS functions
 - No multilevel circuit implementations in ROM (without external connections from output to input). PAL has outputs from OR terms as internal inputs to all AND terms, making implementation of multi-level circuits easier.
- Disadvantage
 - ROM guaranteed to implement any M functions of N inputs. PAL may have too few inputs to the OR gates.

Programmable Array Logic Example


- 4-input, 4-output PAL with fixed, 3-input OR terms
- What are the equations for F1 through F4?

$$F1 = \overline{\overline{A}}\overline{\overline{B}} + \overline{C}$$

$$F2 = \overline{A}B\overline{C} + AC + A\overline{B}$$

$$F3 =$$

$$F4 =$$

 

Programmable Array Logic

- **Design requires fitting functions within the limited number of ANDs per OR gate**
- **Single function optimization is the first step to fitting**
- **Otherwise, if the number of terms in a function is greater than the number of ANDs per OR gate, then factoring is necessary**

Programmable Array Logic Example

- Equations: $F1 = A\bar{B}\bar{C} + \bar{A}B\bar{C} + \bar{A}\bar{B}C + ABC$
 $F2 = AB + BC + AC$

- F1 must be factored since four terms

- Factor out last two terms as W


Product term	AND Inputs					Outputs
	A	B	C	D	W	
1	0	0	1	—	—	$W = \bar{A}\bar{B}C + ABC$
2	1	1	1	—	—	
3	—	—	—	—	—	
4	1	0	0	—	—	$F1 = X = \bar{A}\bar{B}\bar{C} + \bar{A}B\bar{C} + W$
5	0	1	0	—	—	
6	—	—	—	—	1	
7	1	1	—	—	—	$F2 = Y = AB + BC + AC$
8	—	1	1	—	—	
9	1	—	1	—	—	
10	—	—	—	—	—	
11	—	—	—	—	—	
12	—	—	—	—	—	

Programmable Array Logic Example

$$W = \overline{\overline{A}}\overline{\overline{B}}\overline{\overline{C}} + \overline{A}\overline{B}\overline{C}$$

$$F1 = X = \overline{\overline{A}}\overline{\overline{B}}\overline{\overline{C}} + \overline{A}\overline{B}\overline{C} + W$$
 
$$F2 = Y = \overline{A}\overline{B} + \overline{B}\overline{C} + \overline{A}\overline{C}$$



Programmable Logic Array (PLA)


- Compared to a ROM and a PAL, a PLA is the most flexible having a programmable set of ANDs combined with a programmable set of ORs.
- Advantages
 - A PLA can have large N and M permitting implementation of equations that are impractical for a ROM (because of the number of inputs, N, required)
 - A PLA has all of its product terms connectable to all outputs, overcoming the problem of the limited inputs to the PAL Ors
 - Some PLAs have outputs that can be complemented, adding POS functions

Programmable Logic Array (PLA)

■ Disadvantages

- Often, the product term count limits the application of a PLA.
- Two-level multiple-output optimization is required to reduce the number of product terms in an implementation, helping to fit it into a PLA.
- Multi-level circuit capability available in PAL not available in PLA. PLA requires external connections to do multi-level circuits.

Programmable Logic Array Example

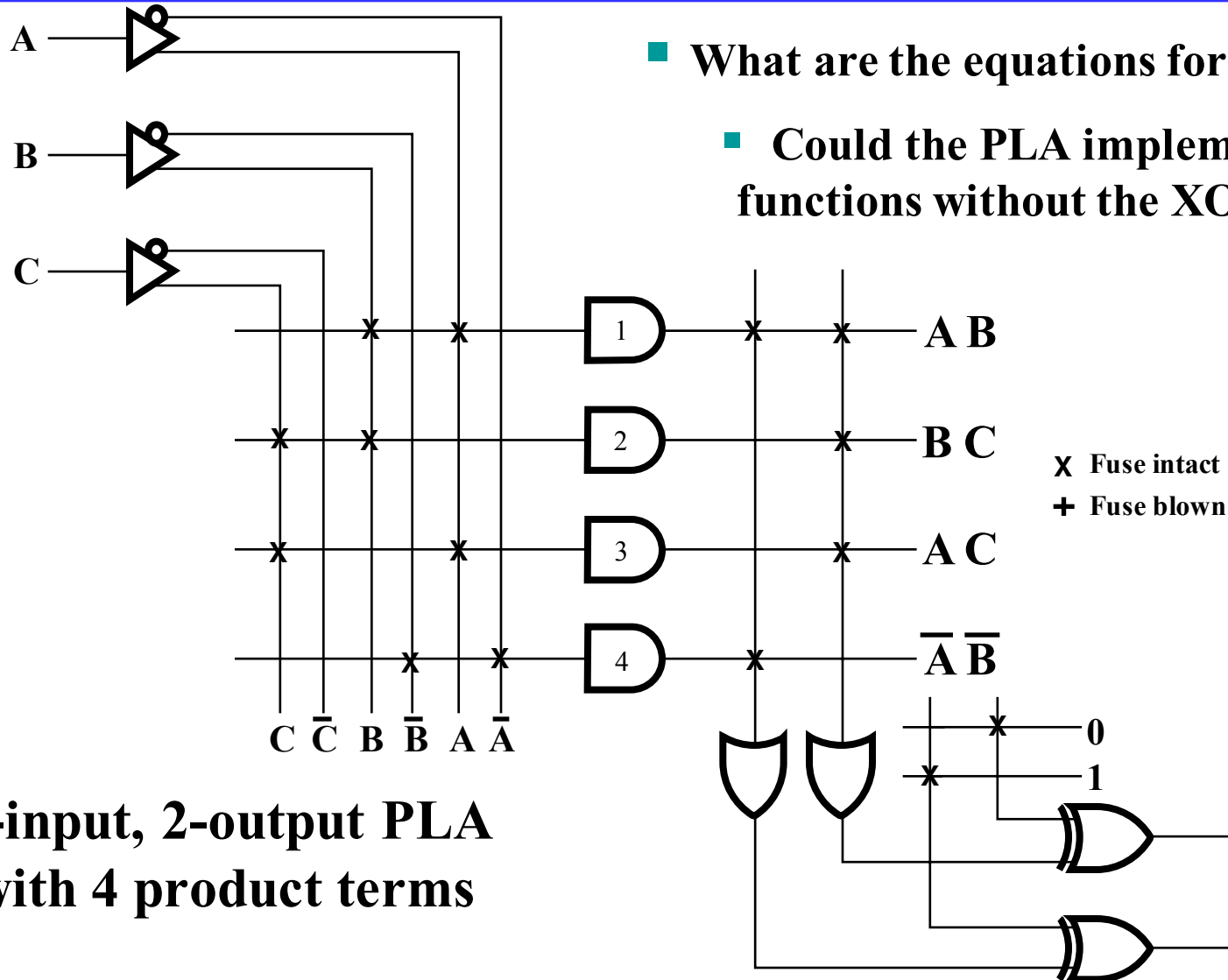

- 3-input, 2-output PLA with 4 product terms

■ What are the equations for F_1 and F_2 ?



■ Could the PLA implement the functions without the XOR gates?

Programmable Logic Array

- The set of functions to be implemented must fit the available number of product terms
- The number of literals per term is less important in fitting
- Since output inversion is available, terms can implement either a function or its complement
- For small circuits, K-maps can be used to visualize product term sharing and use of complements
 - The best approach to fitting is multiple-output, two-level optimization (which has not been discussed)
- For larger circuits, software is used to do the optimization including use of complemented functions

Programmable Logic Array Example

  - K-map specification
- How can this be implemented with four terms?



- Complete the programming table

$$F_1 = \bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}\bar{C}$$

$$\bar{F}_1 = AB + AC + BC + \bar{A}\bar{B}\bar{C}$$


$$F_2 = AB + AC + BC$$

$$\bar{F}_2 = \bar{A}\bar{C} + \bar{A}\bar{B} + \bar{B}\bar{C}$$

PLA programming table

				Outputs		
				(C)	(T)	
	Product term	A	B	C	F_1	F_2
AB	1	1	1	–	1	1
AC	2	1	–	1	1	1
BC	3	–	1	1	1	1
$\bar{A}\bar{B}\bar{C}$	4	0	0	0	1	–

Programmable Logic Array Example

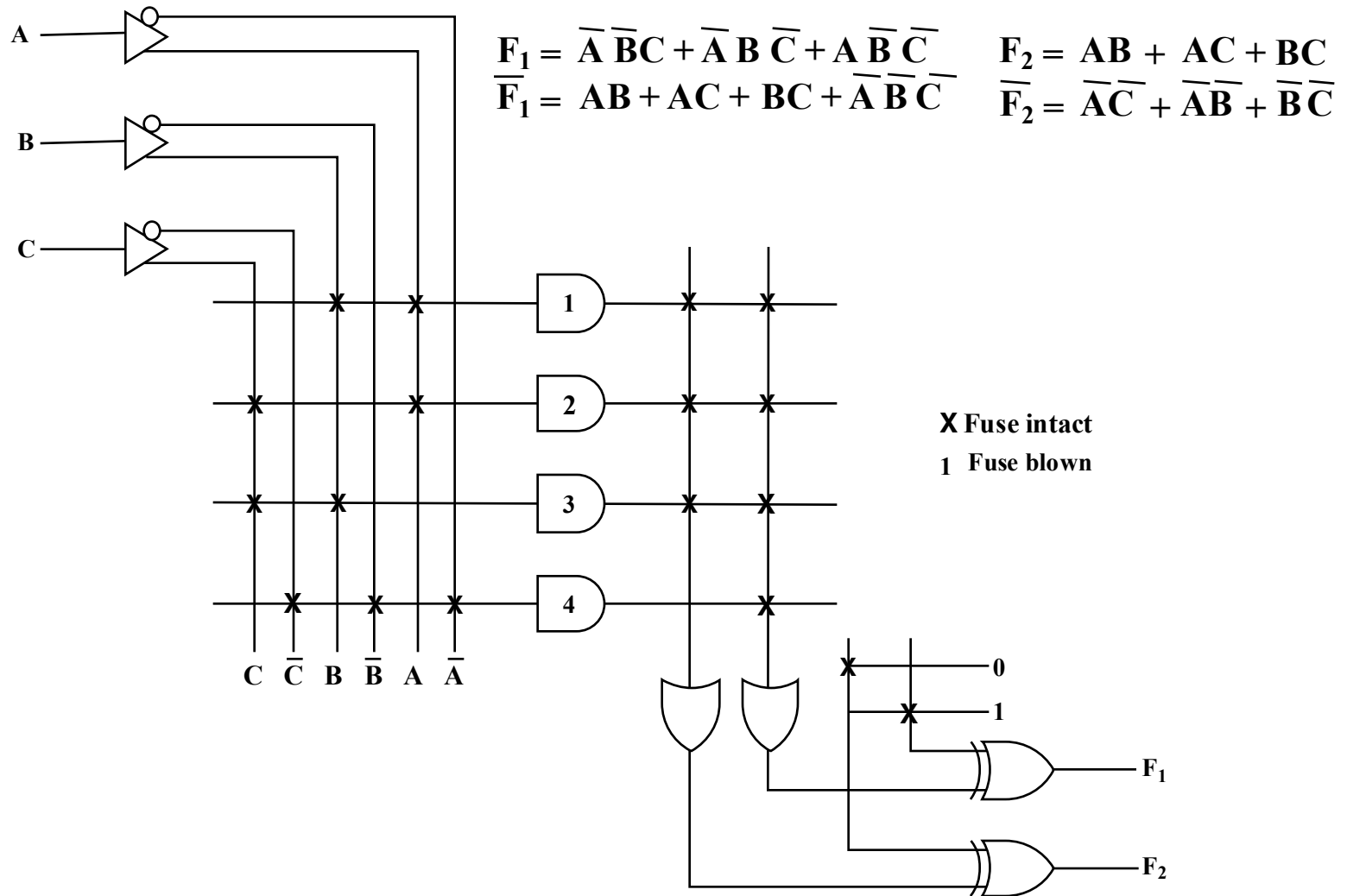

Assignments

- 6-9, 6-10, 6-12, 6-20