
Logic and Computer Design Fundamentals

Chapter 6 – Selected Design Topics

Part 1 – The Design Space

Yueming Wang (王跃明)

ymingwang@zju.edu.cn

2017

College of Computer Science, Zhejiang University

Qiusi Academy for Advanced Studies, Zhejiang University


Overview

- **Part 1 – The Design Space**
 - **Integrated Circuits**
 - **Levels of Integration**
 - **CMOS Circuit Technology**
 - **CMOS Transistor Models**
 - **Circuits of Switches**
 - **Fully Complementary CMOS Circuits**
 - **Technology Parameters**
- **Part 2 – Propagation Delay and Timing**
- **Part 3 – Asynchronous Interactions**
- **Part 4 - Programmable Implementation Technologies**


Integrated Circuits

- **Integrated circuit (informally, a “chip”) is a semiconductor crystal (most often silicon) containing the electronic components for the digital gates and storage elements which are interconnected on the chip.**
- **Terminology - Levels of chip integration**
 - *SSI (small-scale integrated)* - fewer than 10 gates
 - *MSI (medium-scale integrated)* - 10 to 100 gates
 - *LSI (large-scale integrated)* - 100 to thousands of gates
 - *VLSI (very large-scale integrated)* - thousands to 100s of millions of gates

MOS Transistor

 


MOS Transistor

 

Switch Models for MOS Transistors

 
- **n-Channel – Normally Open (NO) Switch Contact**



Symbol




Switch Model:

 

Simplified
Switch Model

 
- **p-Channel – Normally Closed (NC) Switch Contact**



Symbol




Switch Model

 


Simplified
Switch Model

Circuits of Switch Models

- **Series**

 


- **Parallel**

 

Fully-Complementary CMOS Circuit

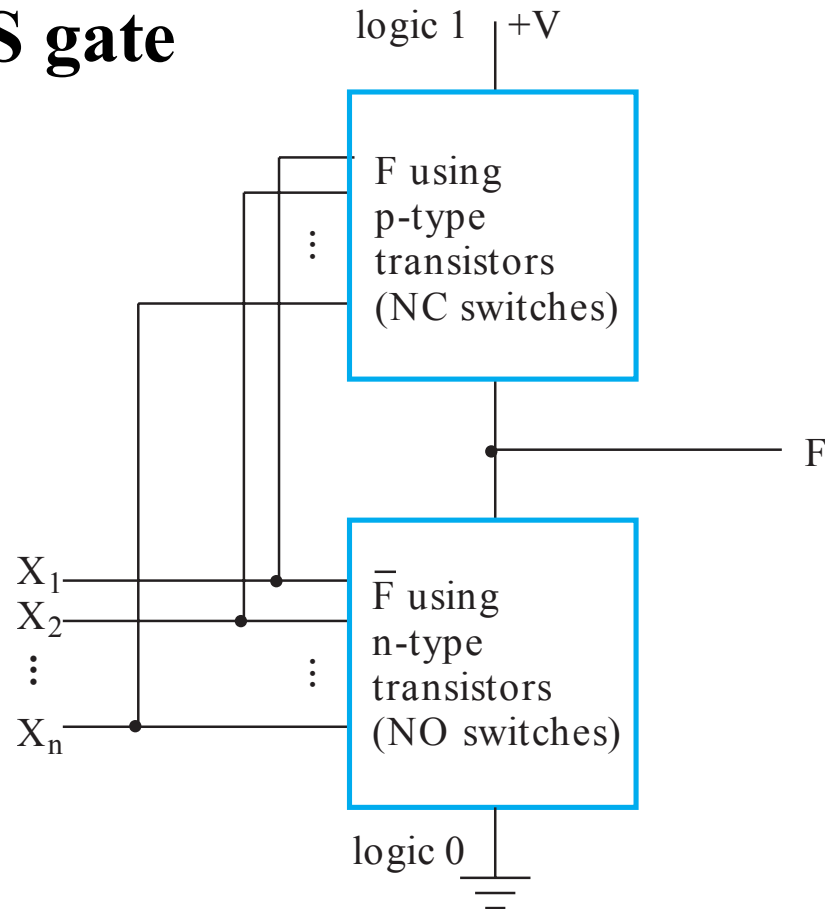- **Circuit structure for fully-complementary CMOS gate**



General Structure


CMOS Circuit Design Example

- Find a CMOS gate with the following function: $F = \bar{X} Z + \bar{Y} Z = (\bar{X} + \bar{Y})Z$

- Beginning with F0, and using \bar{F}


$$\text{F0 Circuit: } \bar{F} = X Y + \bar{Z}$$

 - The switch model circuit in terms of NO switches:



CMOS Circuit Design Example

 - The switch model circuit for F1 in terms of NC contacts is the dual of the switch model circuit for F0:




- The function for this circuit is:

$$\text{F1 Circuit: } F = (\bar{X} + \bar{Y}) Z$$

which is the correct F.

CMOS Circuit Design Example

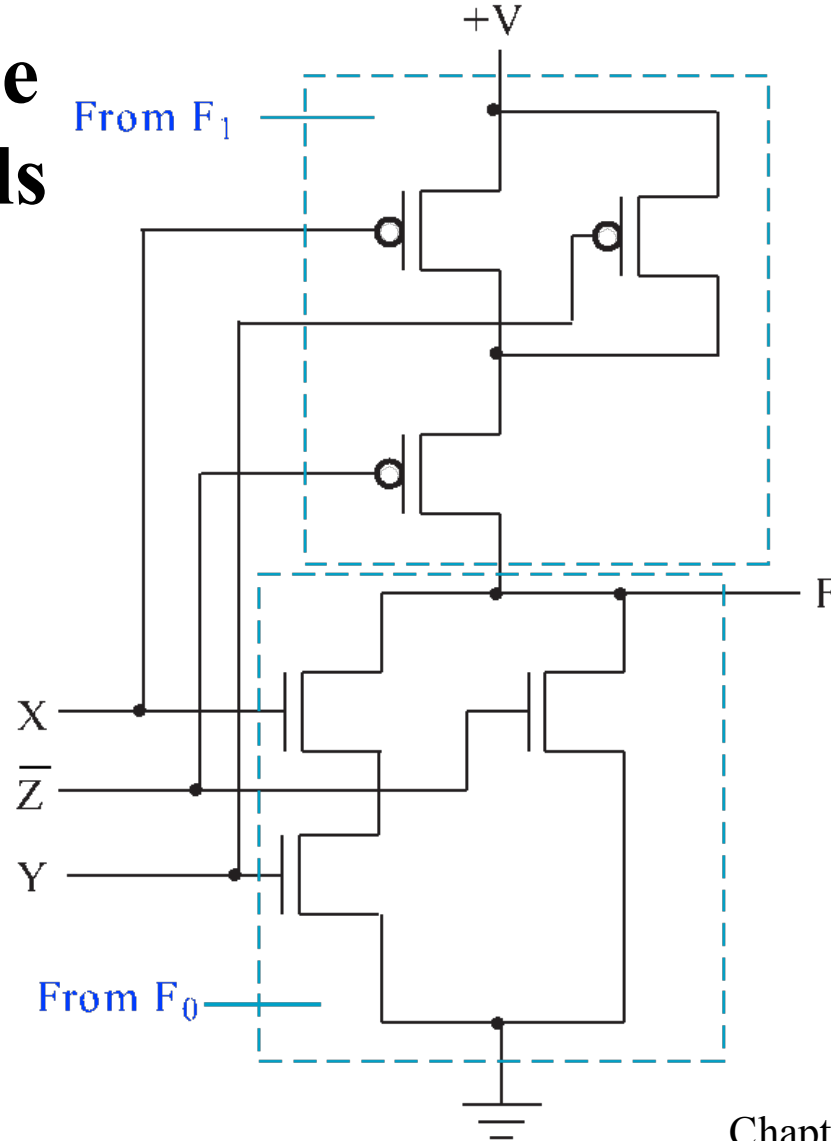- Replacing the switch models with CMOS transistors; note input \bar{Z} must be used.



Technology Parameters

- **Specific gate implementation technologies are characterized by the following parameters:**
 - ***Fan-in*** – the number of inputs available on a gate
 - ***Fan-out*** – the number of standard loads driven by a gate output
 - ***Logic Levels*** – the signal value ranges for 1 and 0 on the inputs and 1 and 0 on the outputs (see Figure 1-1)
 - ***Noise Margin*** – the maximum external noise voltage superimposed on a normal input value that will not cause an undesirable change in the circuit output
 - ***Cost for a gate*** - a measure of the contribution by the gate to the cost of the integrated circuit
 - ***Propagation Delay*** – The time required for a change in the value of a signal to propagate from an input to an output
 - ***Power Dissipation*** – the amount of power drawn from the power supply and consumed by the gate